

EE2013

NON-LINEAR CIRCUIT ANALYSIS

LECTURE 14: THE BJT

Instructors: Alex Jaeger, Anthony Wall
Coordinator: Prof. Pádraig Cantillon-Murphy

LECTURE SCHEDULE

Thursdays 11am-1pm
(with short break)

Back to usual this Thursday, 3rd March

LECTURE NOTES

<https://www.jaeger.ie/ee2013/lec14>

Uploaded after lecture takes place

QUESTIONS?


Just ask whenever it comes to you!

OR:


anthony.wall@mcci.ie on Email, Teams or Canvas

1 Review from last time

The MOSFET gate capacitance can have a significant impact on the response of the device in switching applications. For a MOSFET with a threshold voltage, V_T , C_{GS} can result in measurable delay on turn-on. A typical power MOSFET might have $C_{GS} \approx 1\text{-}10\text{ nF}$ so that even for circuits switching in the kHz range with significant input resistance, delays at turn-on will inevitably occur.

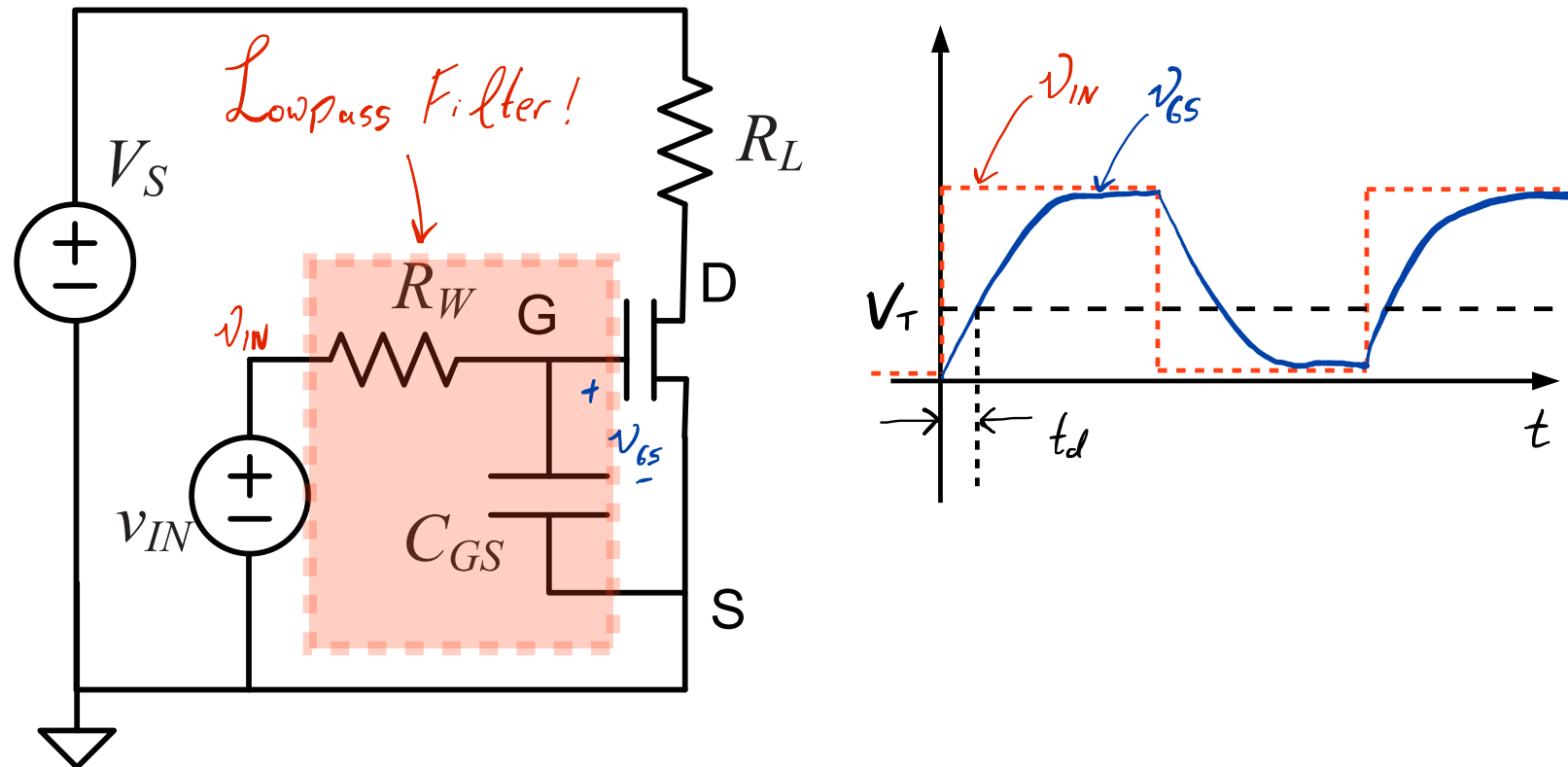

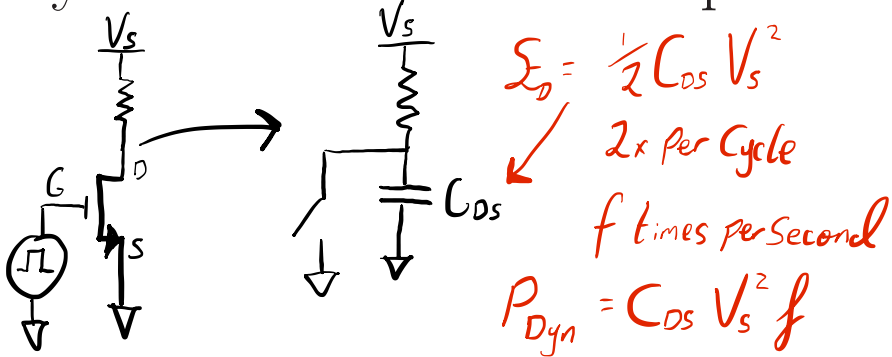As well as C_{GS} , there is also significant capacitance between the MOSFET drain and source, C_{DS} , which leads to dynamic power dissipation on switching. In a simple digital logic inverter operating at 50% duty cycle, the total power losses given below includes both dynamic and static dissipation.



$$E_D = \frac{1}{2} C_{DS} V_s^2$$

✓ 2x Per Cycle
f times per Second

$$P_{DYN} = C_{DS} V_s^2 f$$

Total Power Dissipation:



$$P_D = P_{STATIC} + P_{DYN}$$

$$P_D = \frac{V_s^2}{2(R_L + R_{ON})} + C_{DS} V_s^2 f$$

2 The Bipolar Junction Transistor (BJT)

A second type of transistor is the bipolar junction transistor. Its circuit symbol and large-signal model are shown here. It finds application in demanding analogue circuits, especially for very-high-frequency applications, such as radio-frequency circuits for wireless systems.

Remember MOSFET:

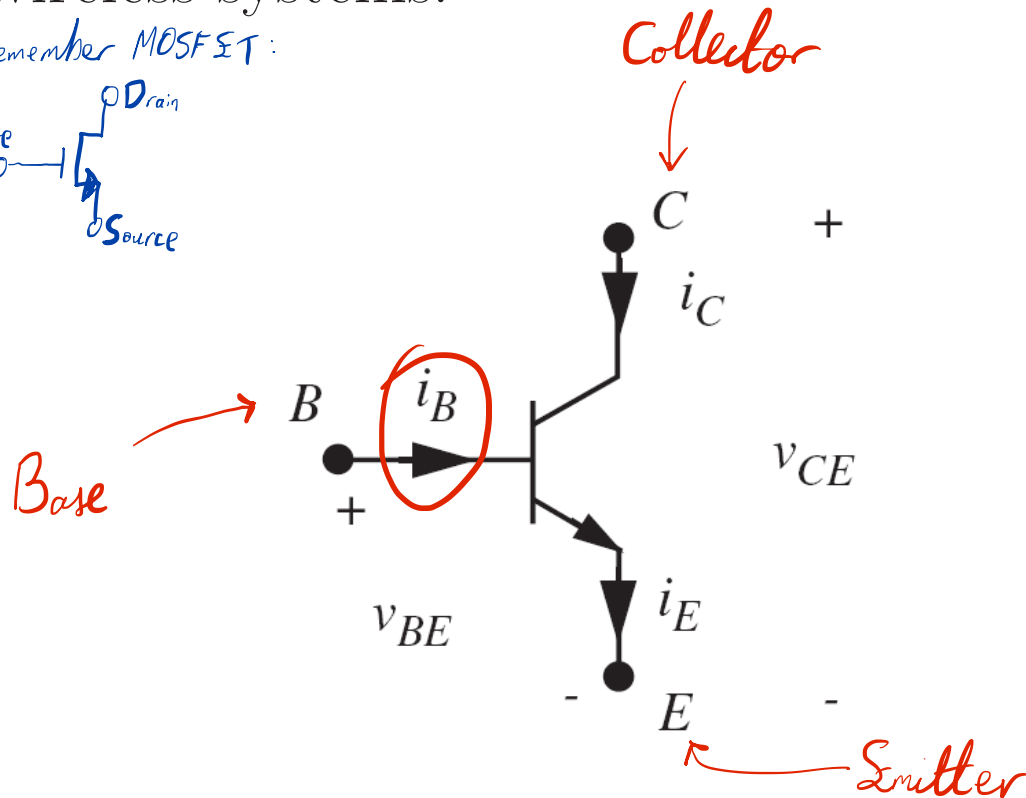
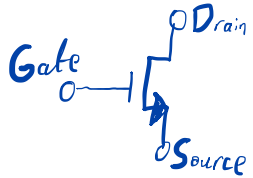


CIRCUIT SYMBOL FOR BJT


2 The Bipolar Junction Transistor (BJT)

A second type of transistor is the bipolar junction transistor. Its circuit symbol and large-signal model are shown here. It finds application in demanding analogue circuits, especially for very-high-frequency applications, such as radio-frequency circuits for wireless systems.

Remember MOSFET:

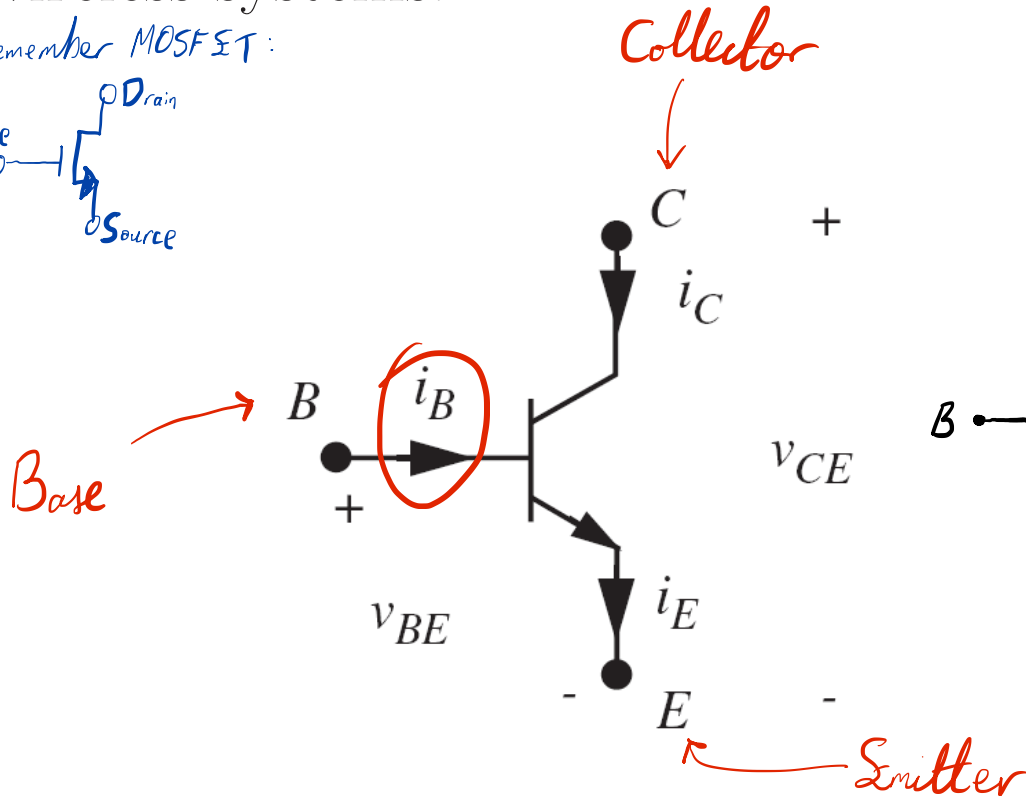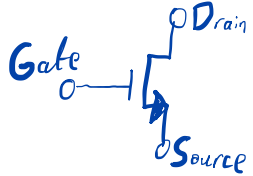


CIRCUIT SYMBOL FOR BJT

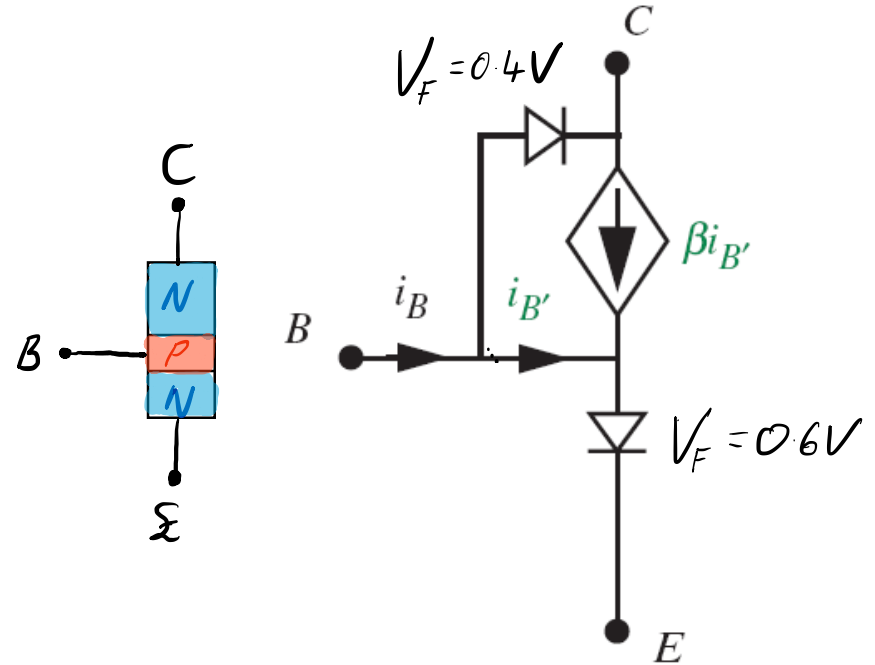

LARGE SIGNAL MODEL

Reset

RUN / Stop

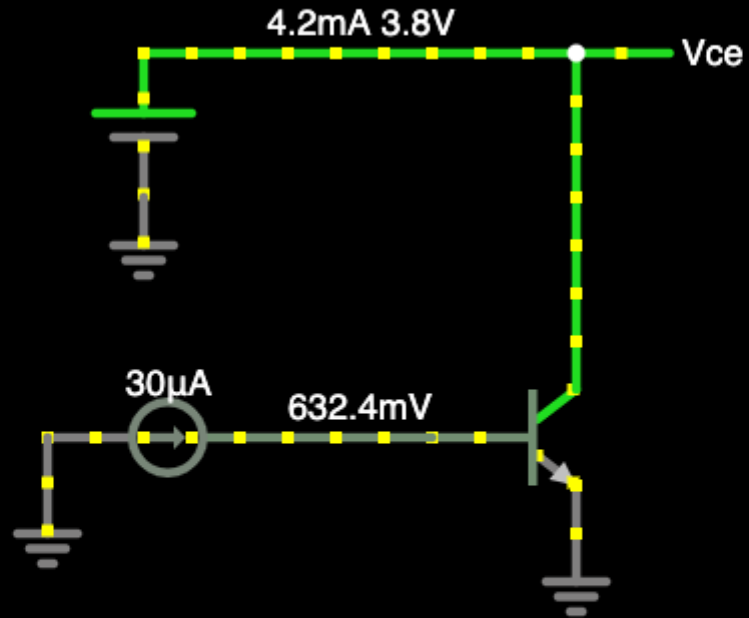

Simulation Speed
< [Slider] >

Current Speed
< [Slider] >

Power Brightness
< [Slider] >

Current Circuit:

V_{ce}
< [Slider] >


I_b
< [Slider] >

Beta
< [Slider] >

$t = 65\ \mu\text{s}$
time step = $5\ \mu\text{s}$


In the active region (where the device normally operates), the piecewise linear model for the BJT is as follows:
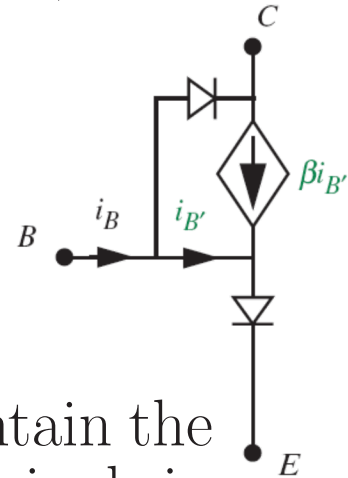
$$i_C = \begin{cases} \beta i_B & \text{if } i_B > 0 \text{ and } v_{CE} > v_{BE} - 0.4\text{V} \\ 0 & \text{otherwise} \end{cases}$$



The second condition on v_{CE} and v_{BE} is necessary to maintain the internal diode between the base (B) and collector (C) terminals in reverse bias. Once this condition is satisfied, a simpler model can be used, shown below, where the internal potential drop across the base-emitter diode is approximately 0.6 V. The large signal model shown above only apply in the forward active region of operation.

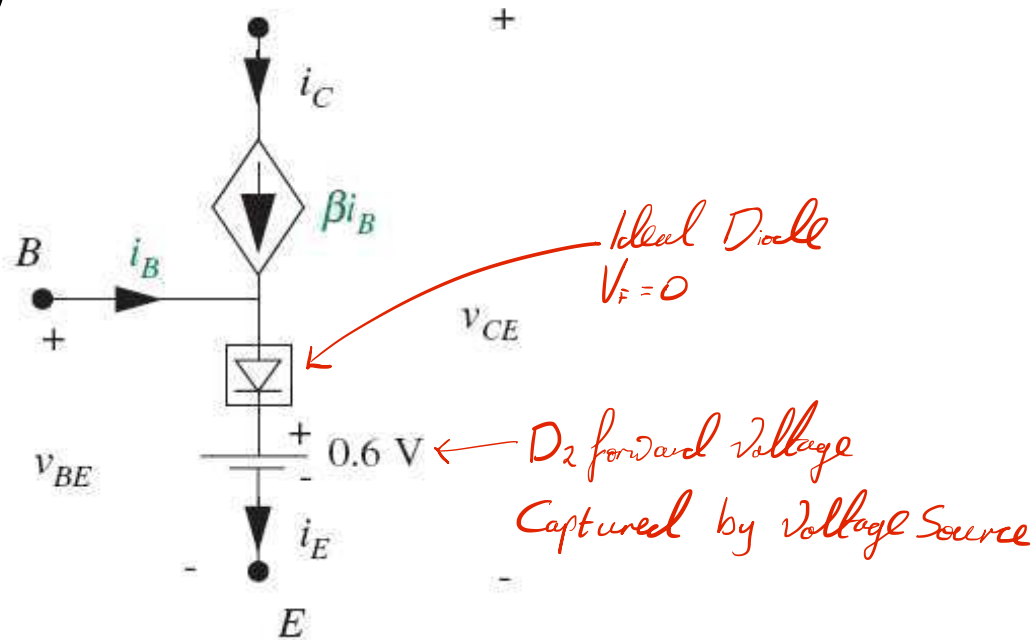$i_B \approx i_B'$
 D₁ Reverse Biased
 ↓
Ignore!



SIMPLIFIED LARGE SIGNAL MODEL

The emitter (E) current, i_E , is given by KCL:

$$i_E = i_C + i_B$$

$$i_E = \beta i_B + i_B = i_B (\beta + 1)$$


Usually $\beta \gg 1$:

$$i_E \approx i_B (\beta)$$


$$i_E \approx i_C$$

3 The Common Emitter BJT Amplifier

The common emitter amplifier resembles the MOSFET common source amplified based on a BJT. This BJT amplifier configuration is called a common emitter amplifier since the emitter terminal of the BJT is common across the input and output ports. Using the piecewise-linear model for the BJT, we will determine the relationship between v_O and v_{IN} , assuming that the BJT device is operating in its active region.

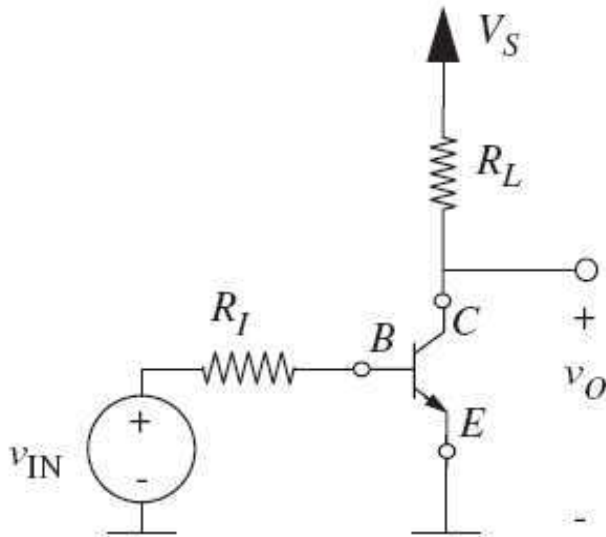


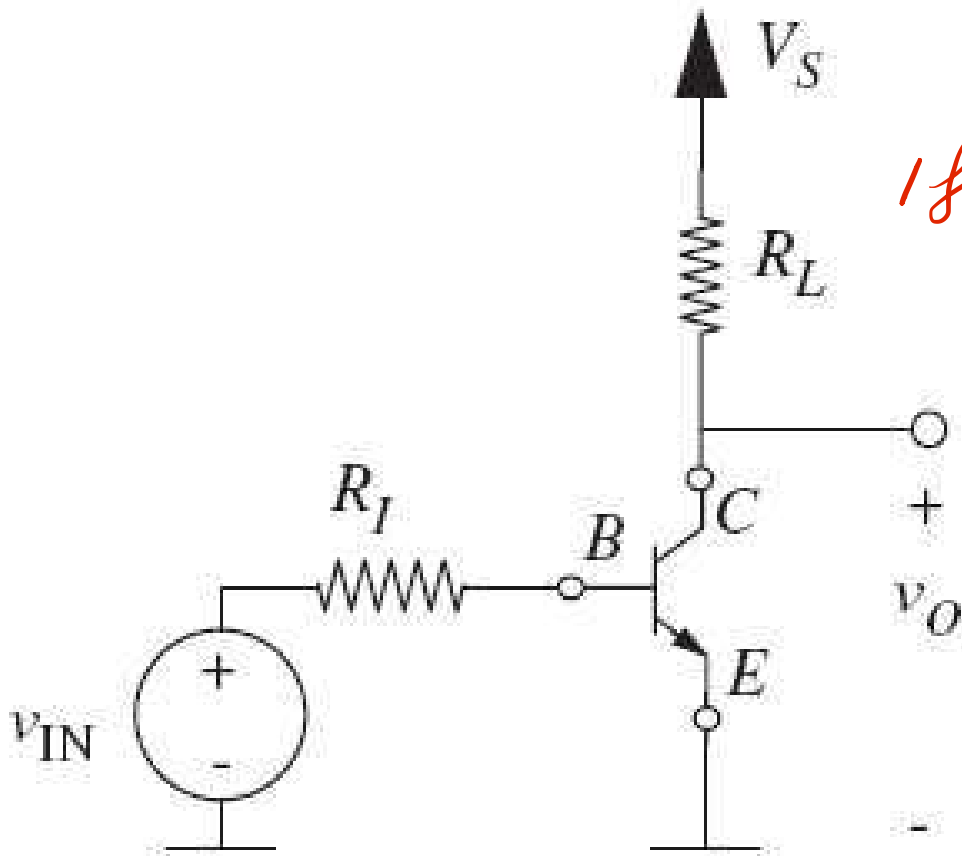- If $v_{IN} \uparrow$
- $V_{R_I} \uparrow$ since v_{BE} is constant
- $i_{R_I} \uparrow$ (Ohm's law)
- $i_C \uparrow$ since $i_C = \beta i_B$
- $v_{R_L} \uparrow$ due to i_C
- $v_O \downarrow$ due to v_{R_L}



If: $V_{CE} > V_{BE} - 0.4$


$\times i_B > 0$

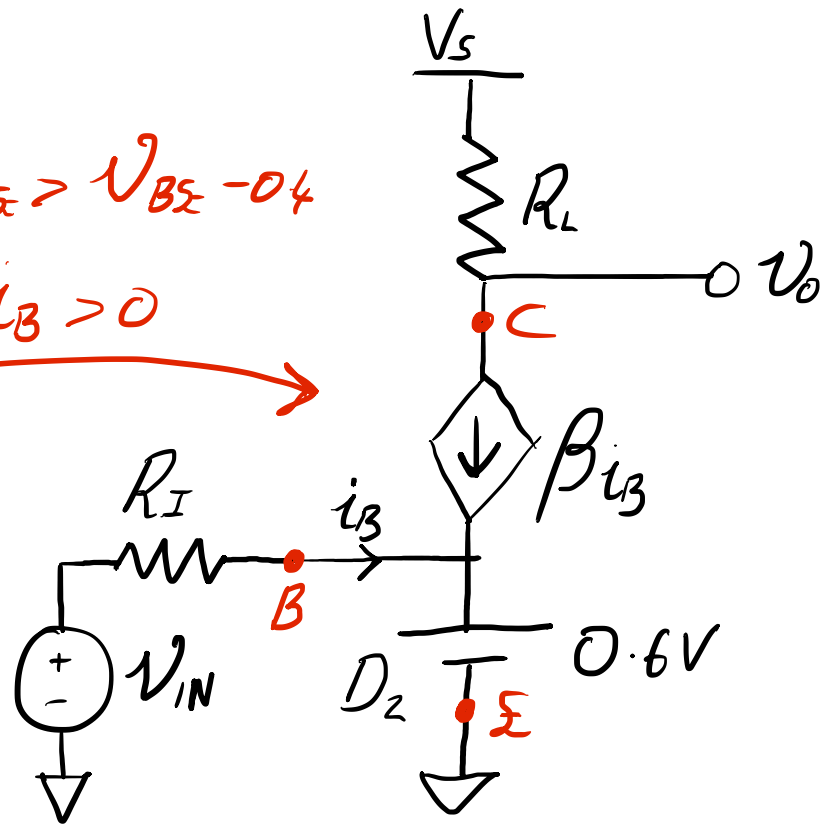

$\Rightarrow V_{BE} \approx 0.6V$ always

$$V_O = V_S - i_C R_L = V_S - (\beta i_B) R_L$$
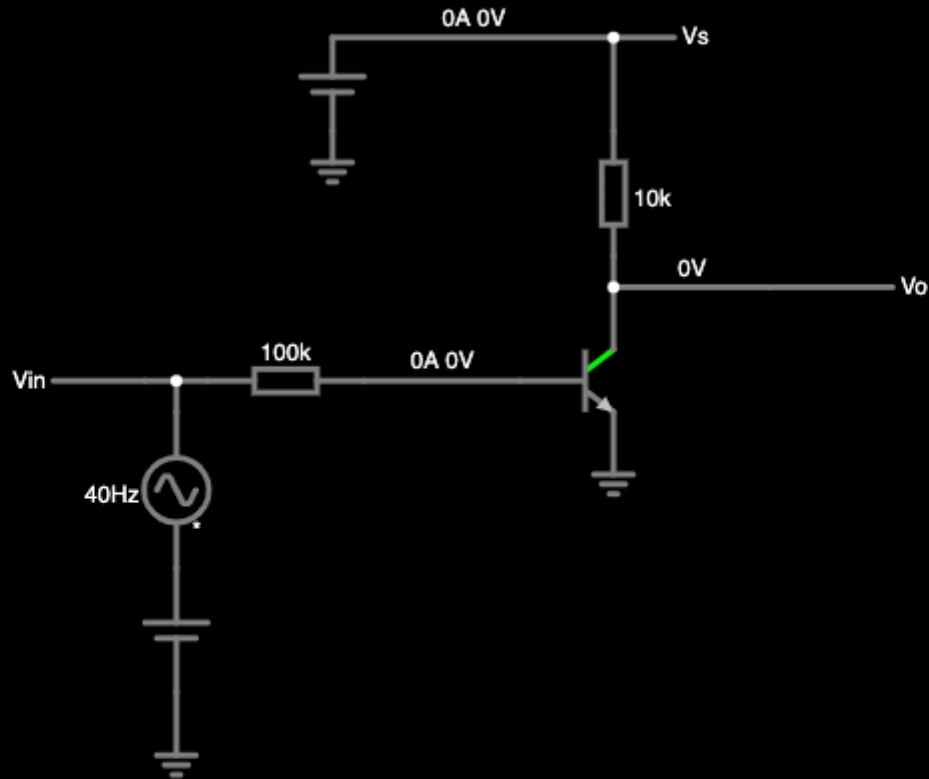
$$V_O = V_S - \beta R_L \left(\frac{V_{IN} - 0.6}{R_I} \right)$$



Reset RUN / Stop

Simulation Speed < [Slider] >

Current Speed < [Slider] >

Power Brightness < [Slider] >

Current Circuit:

V_s < [Slider] >

V_{in_DC} < [Slider] >

V_{in_pk} < [Slider] >

R_{in} < [Slider] >

R_L < [Slider] >

Max=0 V
[Scope Plot Area]

Max=0 V wire
[Scope Plot Area]

t = 0 s
time step = 5 μ s

3.1 Numerical Example


We will analyse the common emitter amplifier for the following values; $R_I = 100 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, $\beta = 100$, and $V_S = 10 \text{ V}$.

$$\begin{aligned}v_o &= V_S - \beta R_L \frac{(v_{IN} - 0.6)}{R_I} \\&= 10 - (100)(10 \times 10^3) \frac{(v_{IN} - 0.6)}{100 \times 10^3} \\&= 10 - 10v_{IN} + 10(0.6)\end{aligned}$$

Inverting! $v_o = 16 \ominus 10v_{IN}$

$$v_o = 16 - 10v_{IN}$$

Two Conditions for Active Region

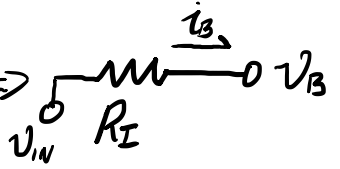① $i_B > 0 \Rightarrow$  $v_B \Rightarrow v_{R_I} > 0$ Remember $v_B = 0.6V$

$\rightarrow v_{IN} > 0.6V$

② For $v_{CE} > v_{BE} - 0.4V$, we note that:

$$v_{CE} = v_O \quad v_{BE} = 0.6V$$

$$v_O > 0.6 - 0.4$$


$$v_O > 0.2V$$

What v_{IN} yields $v_O > 0.2V$?


$$v_O = 16 - 10v_{IN}$$

$$0.2 < 16 - 10v_{IN}$$

$$v_{IN} > 1.58V$$

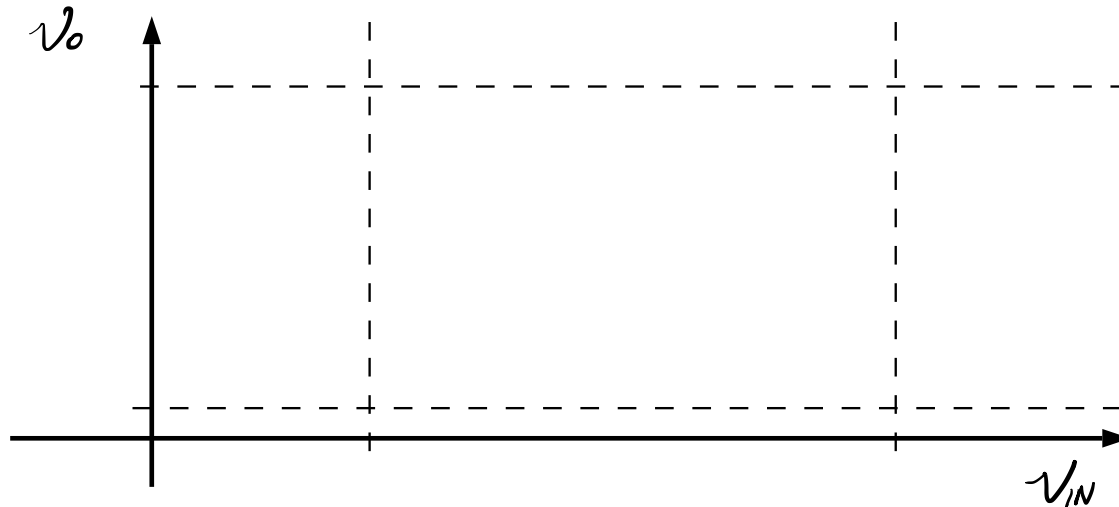

Two Conditions for Active Region

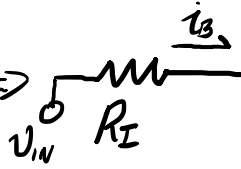① $i_B > 0 \Rightarrow$  $v_B \Rightarrow v_{R_E} > 0$ Remember $v_B = 0.6V$
 $\rightarrow v_{IN} > 0.6V$

② For $v_{CE} > v_{BE} - 0.4V$, we note that:

$$v_{CE} = v_O \quad v_{BE} = 0.6V$$

$$v_O > 0.6 - 0.4$$

$$v_O > 0.2V$$


What v_{IN} yields $v_O > 0.2V$?

$$v_O = 16 - 10v_{IN}$$

$$0.2 < 16 - 10v_{IN}$$

$$v_{IN} > 1.58V$$


Cut-off

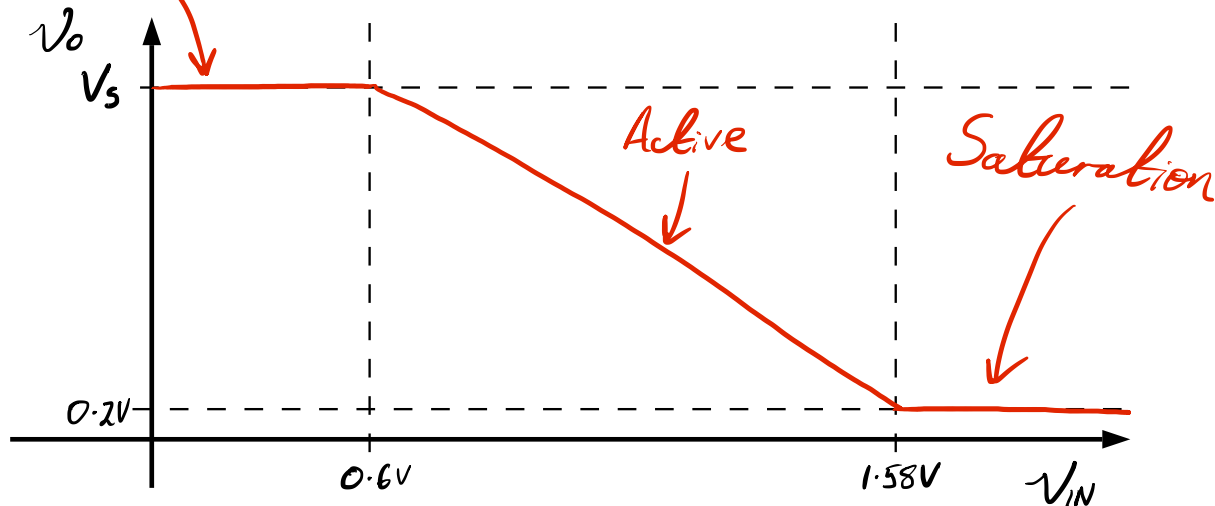


4 Small Signal Model for the BJT

For the small signal model of the BJT, the base-emitter diode can be replaced by a short circuit since we assume that the DC or bias conditions maintain it in forward bias. Therefore the small-signal model for the BJT is simply a linear current-controlled small signal source, as shown below.

Large Signal

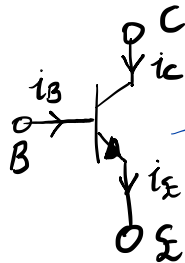

Small Signal

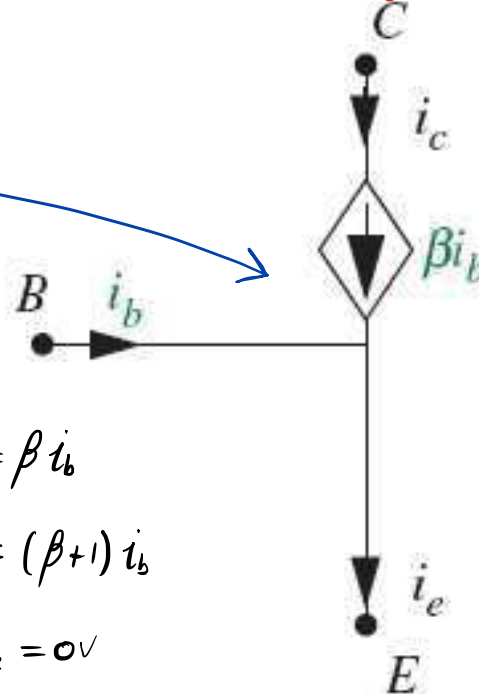


$$i_C = \beta i_B \Rightarrow i_c = \beta i_b$$

$$i_E = (\beta + 1) i_B \Rightarrow i_e = (\beta + 1) i_b$$


$$V_{BE} = 0.6V \Rightarrow v_{be} = 0V$$

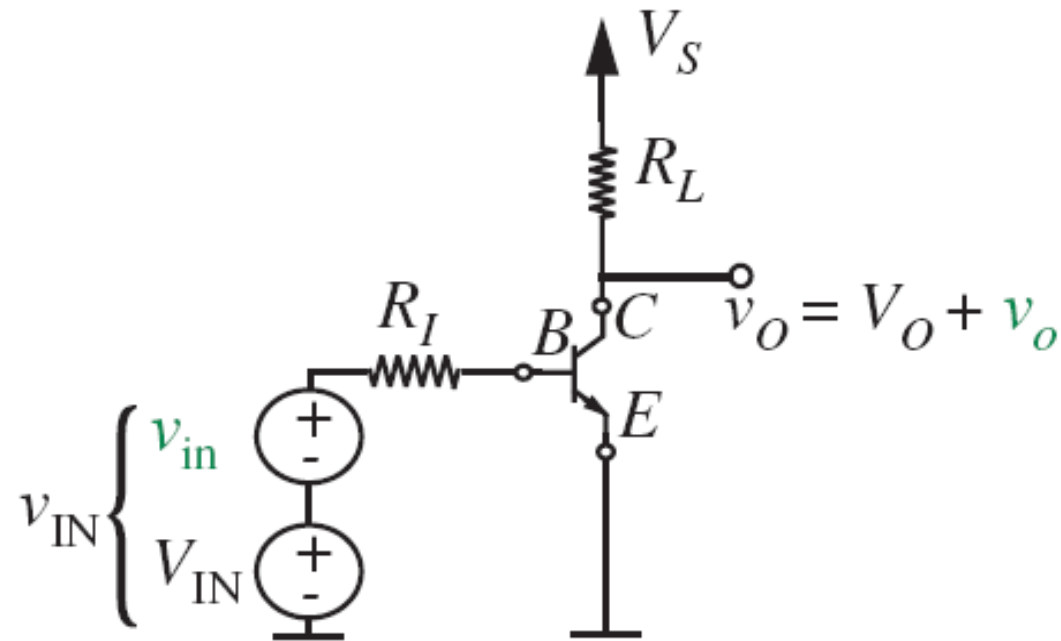To calculate the small-signal output voltage, v_o , replace the BJT with its small signal model and consider the small signal circuit.




The small signal model is shown below:

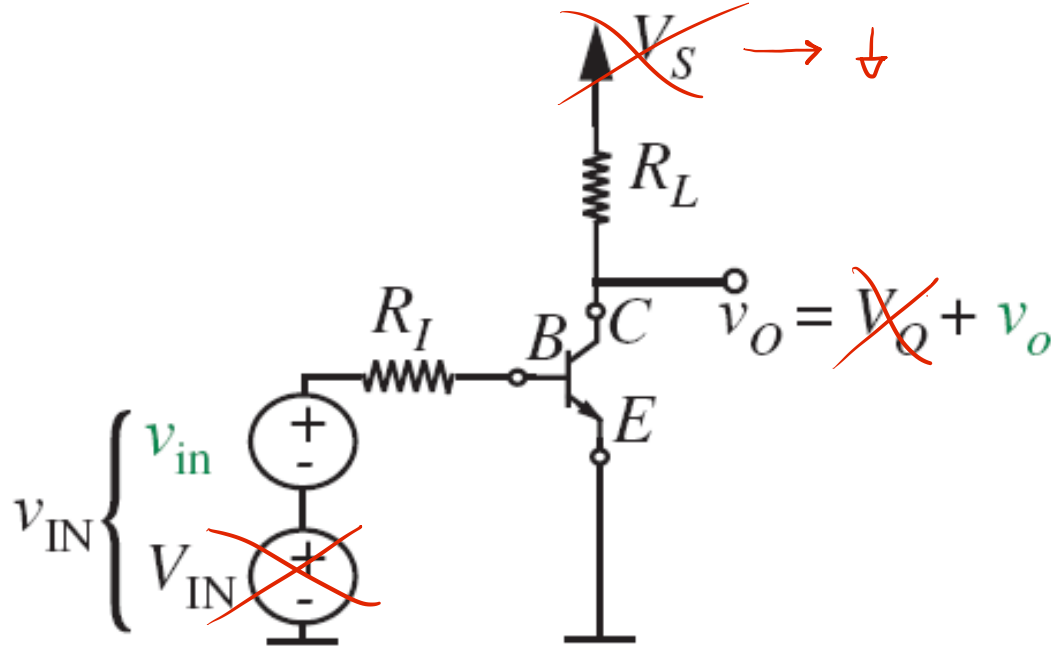To calculate the small-signal output voltage, v_o , replace the BJT with its small signal model and consider the small signal circuit.



The small signal model is shown below:

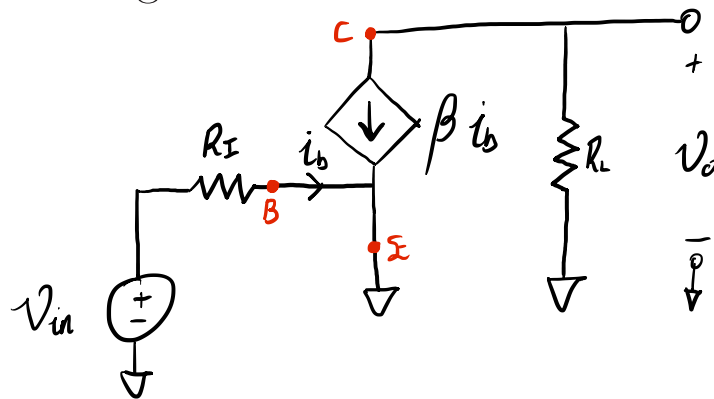

4.1 Example: Small Signal Gain of the Common Emitter Amplifier

We compute the small-signal gain (v_o/v_{in}) for the BJT common emitter amplifier, assuming that the amplifier operates in its active region. Again, $R_I = 100 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, $\beta = 100$, $V_S = 10 \text{ V}$ and the input bias voltage is chosen to be $V_{IN} = 1 \text{ V}$.

Large Signal Reminder : $v_o = 16 - 10 v_{in} = 16 - 10 = 6 \text{ V}$ Active!

$$v_o = V_S - \beta R_L \frac{(v_{in} - 0.6)}{R_I}$$

$$v_o = -i_c R_L =$$

$$v_o = -10 v_{in}$$

The linear small signal response of the common emitter amplifier makes it a good amplifier for high fidelity audio amplifier designs.

4.1 Example: Small Signal Gain of the Common Emitter Amplifier

We compute the small-signal gain (v_o/v_{in}) for the BJT common emitter amplifier, assuming that the amplifier operates in its active region. Again, $R_I = 100 \text{ k}\Omega$, $R_L = 10 \text{ k}\Omega$, $\beta = 100$, $V_S = 10 \text{ V}$ and the input bias voltage is chosen to be $V_{IN} = 1 \text{ V}$.

Large Signal Reminder: $v_o = 16 - 10 v_{in} = 16 - 10 = 6 \text{ V}$ Active!

$$v_o = \cancel{V_S} - \beta R_L \frac{(v_{in} - \cancel{0.6})}{R_I}$$

$$v_o = -\beta \frac{R_L}{R_I} v_{in}$$

OR:

$$v_o = -i_c R_L = -\beta i_b R_L$$

$$v_o = -\beta \left(\frac{v_{in}}{R_I} \right) R_L$$

Substitute above values:

$$v_o = -100 \left(\frac{10}{100} \right) v_{in}$$

Inverting!

$$v_o = -10 v_{in}$$

The linear small signal response of the common emitter amplifier makes it a good amplifier for high fidelity audio amplifier designs.