

EE2013

NON-LINEAR CIRCUIT ANALYSIS

LECTURE 16: THE OPERATIONAL AMPLIFIER

Instructors: Alex Jaeger, Anthony Wall

Coordinator: Prof. Pádraig Cantillon-Murphy

LECTURE SCHEDULE

Thursdays 11am-1pm
(with short break)

Monday 9am-10am slot not used!

LECTURE NOTES

<https://www.jaeger.ie/ee2013/lec16>

Uploaded after lecture takes place

QUESTIONS?


Just ask whenever it comes to you!

OR:


anthony.wall@mcci.ie on Email, Teams or Canvas

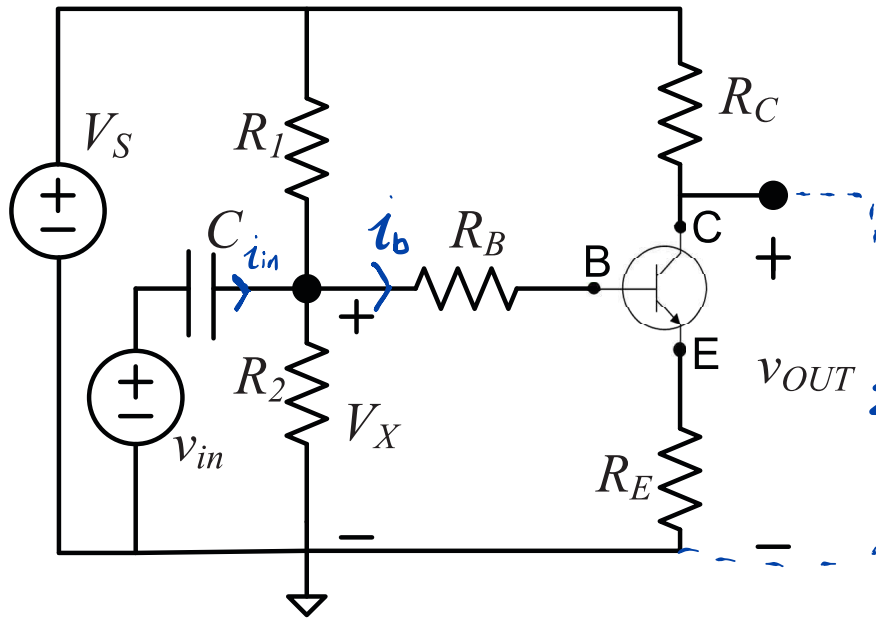1.1 BJT and DC Bias


The DC biasing resistors in the BJT common emitter amplifier ensure that the circuit remains in the *forward active* region of operation.




Large Signal Model

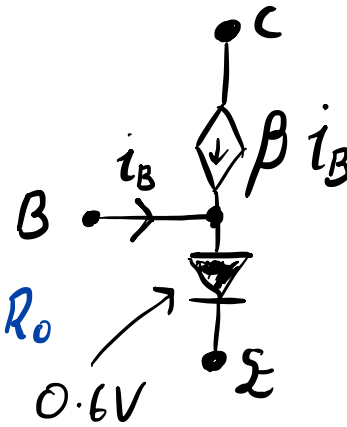

Small Signal Model

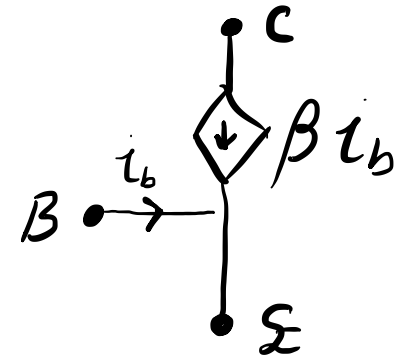

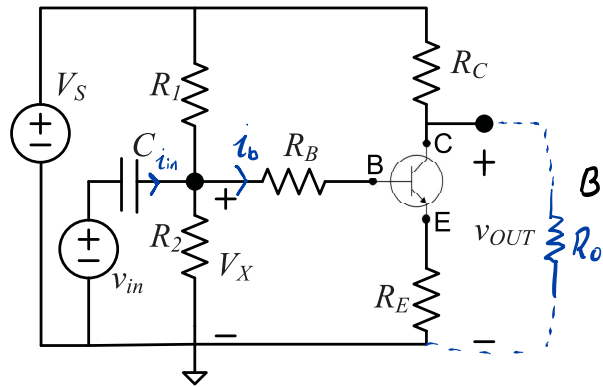1.2 Small Signal Parameters for BJT Common Emitter Amplifier




| Parameter | Value for BJT CE Amplifier |
|--------------------------------|---|
| Small signal voltage gain | $A_v = -R_c / R_E$ |
| Small signal input resistance | $r_{in} = (R_1 // R_2) // (R_B + (\beta + 1) R_E)$ |
| Small signal output resistance | $R_o \approx R_c$ |
| Small signal current gain | $A_i = \frac{i_{out}}{i_b} \cdot \frac{i_b}{i_{in}} = \beta \left(\frac{R_o}{R_c + R_o} \right) \cdot \frac{(R_1 // R_2)}{r_{in}' + (R_1 // R_2)}$ |
| Small signal power gain | $ A_v A_i $ |

2 The Operational-Amplifier

Today, we look at a new device: the operational amplifier, commonly termed the *op-amp*.

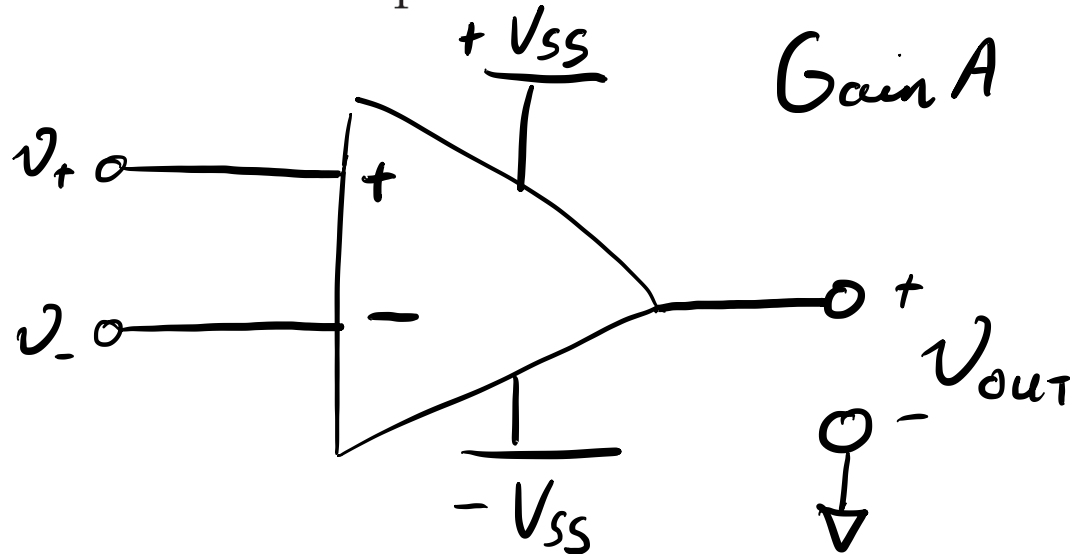
The integrated-circuit operational-amplifier is the fundamental building block for many electronic circuits. An op-amp is simply a very high gain electronic amplifier with a pair of differential inputs. Its functionality comes about through the use of *feedback* around the amplifier as we will show.



The op-amp has the following characteristics:

- Op-amps are typically powered by two DC voltage levels, $+V_{SS}$ and $-V_{SS}$. A typical value for V_{SS} is 15 V. In circuit diagrams, these connections are almost always ignored and not included as it's assumed that the op-amp is powered on during operation.

$$i_+ \approx i_- \approx 0$$

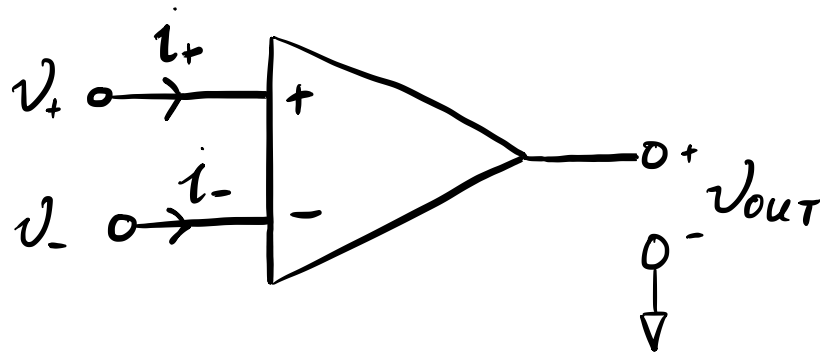


- The op-amp is basically a “three terminal” signal amplifier with two inputs and an output. It is a differential amplifier with very high gain, A , (typically 10^4 to 10^5). The two inputs are known as the non-inverting (v^+) and inverting (v^-) inputs respectively. In the ideal op-amp we assume that the gain A is infinite.

$$v_{out} = A(v^+ - v^-)$$

Very Large!

- In an ideal op-amp no current flows into either input, that is to say, they are voltage-controlled and have infinite input resistance. In a practical op-amp the input current is in the order of pico-amps (10^{-12}) amps, or less.

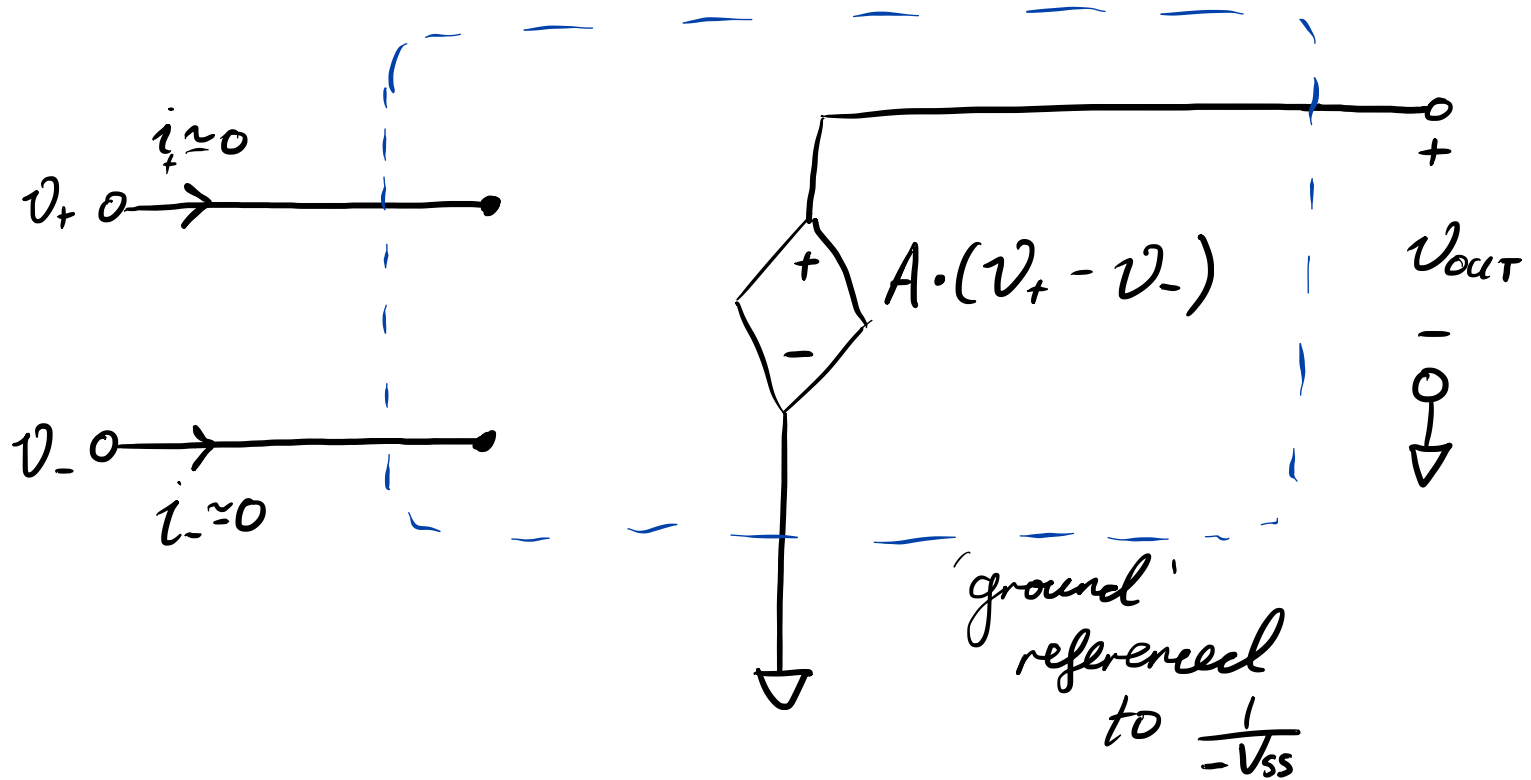
- The output acts as a voltage source, so that it can be modelled as a Thevenin source with a very low source resistance.




3 Characteristics of Op-amps

Op-amps come in many forms and with a bewildering array of specifications. They range in cost from a few cents upwards, depending on the characteristics. These specifications include input impedance, input bias current, output offset voltage, external power requirements *etc.* Higher grade amplifiers are known as precision, or instrumentation amplifiers. The LM741 is the industry standard 741 op-amp wherever possible. Although it was a major step forward in its day, by today's standards it is not a high performance amplifier. Its major advantage is that it costs about \$0.30!

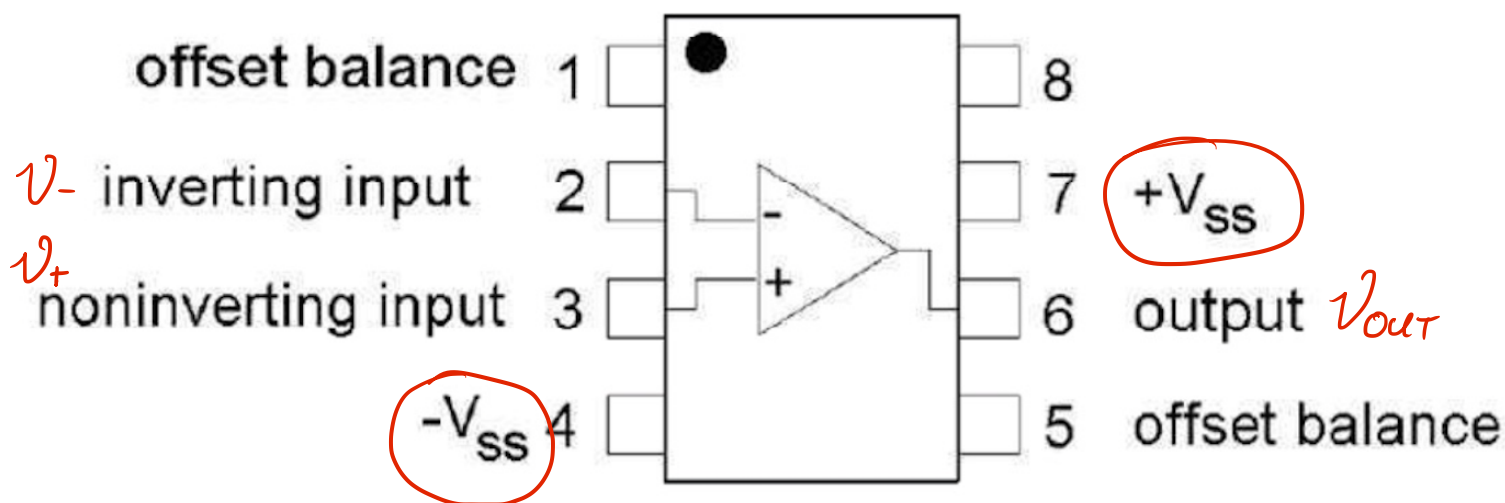Op-amps come in a variety of “packages”. For our laboratory assignment, we will be using the common discrete 8 pin DIP (dual inline package) form. Many op-amps use the same common pin-out for this package as shown below:




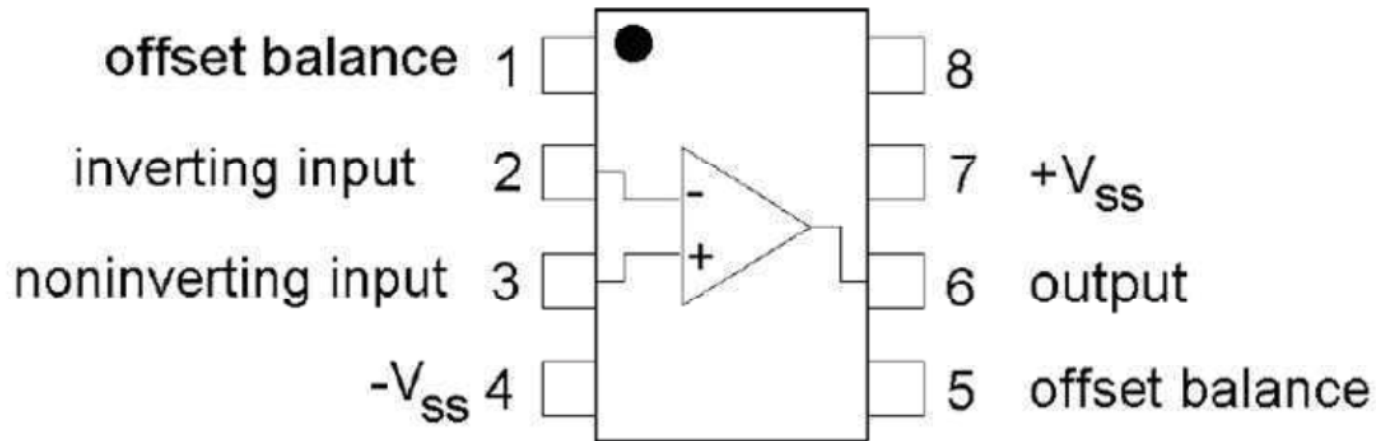

The pins are numbered counter-clockwise from the top left as shown above. (Note that pin 1 is identified by a notch at the top or a dot beside it.) The basic amplifier is connected between pins 2, 3 and 6. The amplifier requires a pair of external supply voltages to operate, typically ± 15 V, as already mentioned. These connections are made to pins 7 (positive) and 4 (negative). Pins 1 and 5 are usually used for optional external offset nulling circuitry - the actual connection is dependent on the type. We will not use this feature in this module.

4 The Unity Gain Buffer

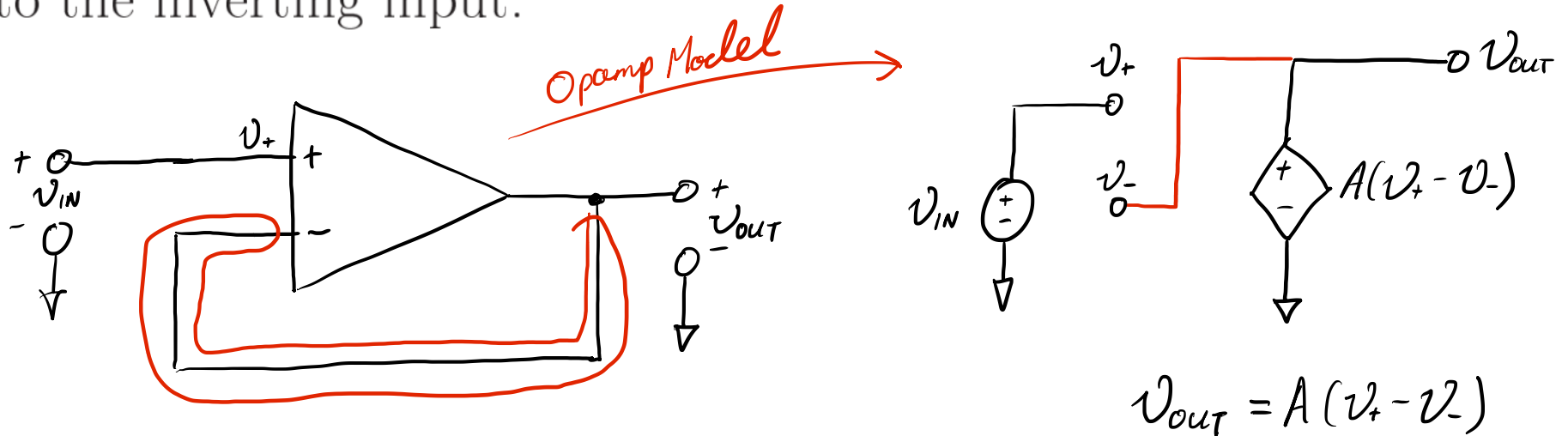The simplest circuit configuration of the op-amp is as a unity gain “buffer” amplifier where the output is connected directly to the inverting input.




Since A is typically 10^4 or higher the transfer relation simplifies as follows:

$$V_{OUT} = A(V_{IN} - V_{OUT})$$


$$V_{OUT} = V_{IN} \frac{A}{1+A} \approx V_{IN}$$

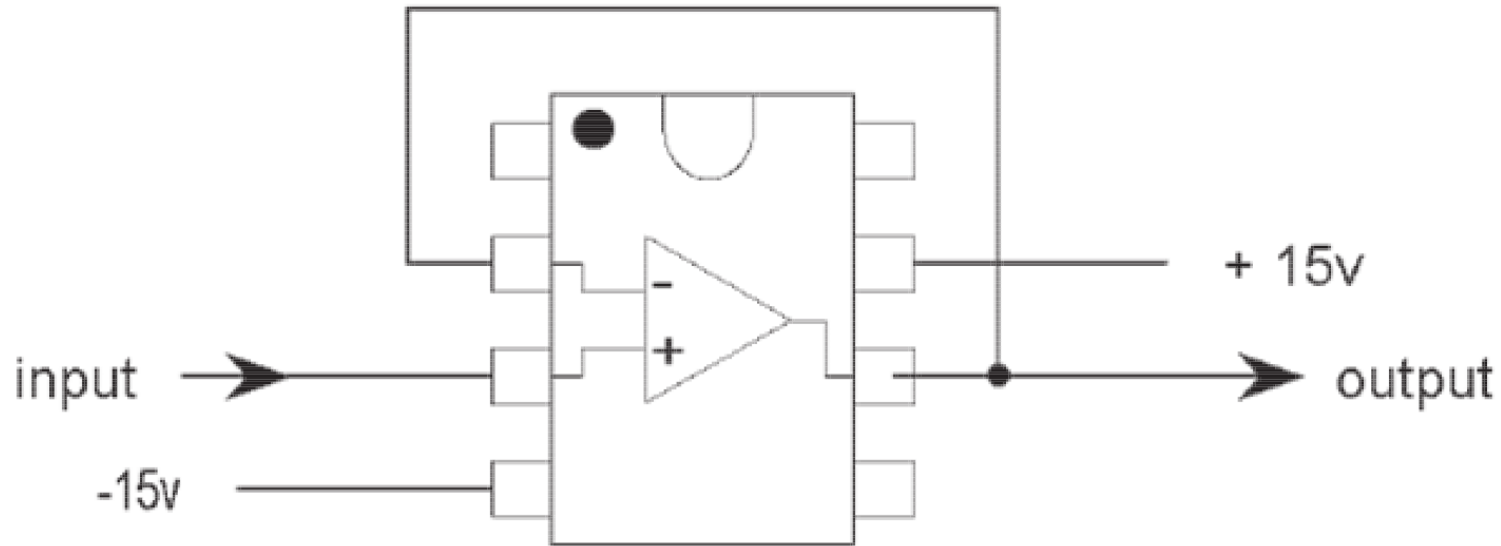
The unity gain amplifier is used commonly to minimize loading on a circuit because it draws no current yet provides a low output resistance output...a highly desirable feature for many circuits.



5 The Non-Inverting Amplifier

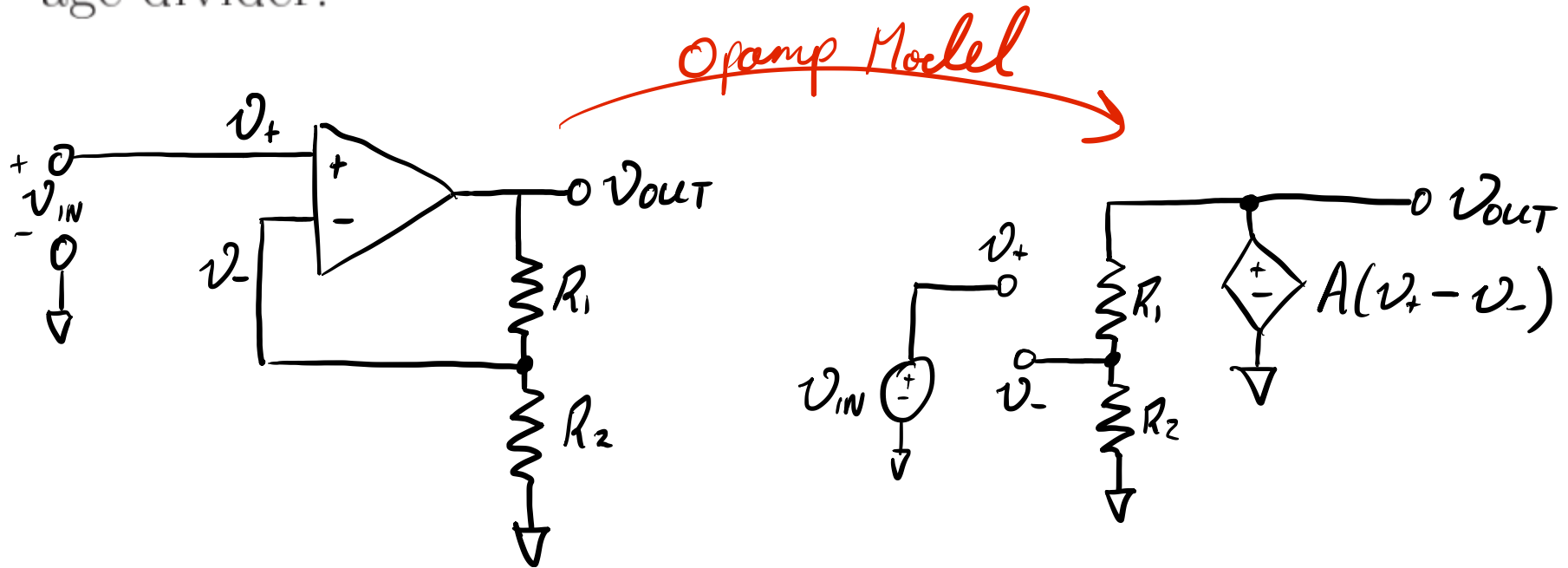The op-amp buffer circuit may be modified to feedback only a fraction of the output voltage by including a two resistor voltage divider.



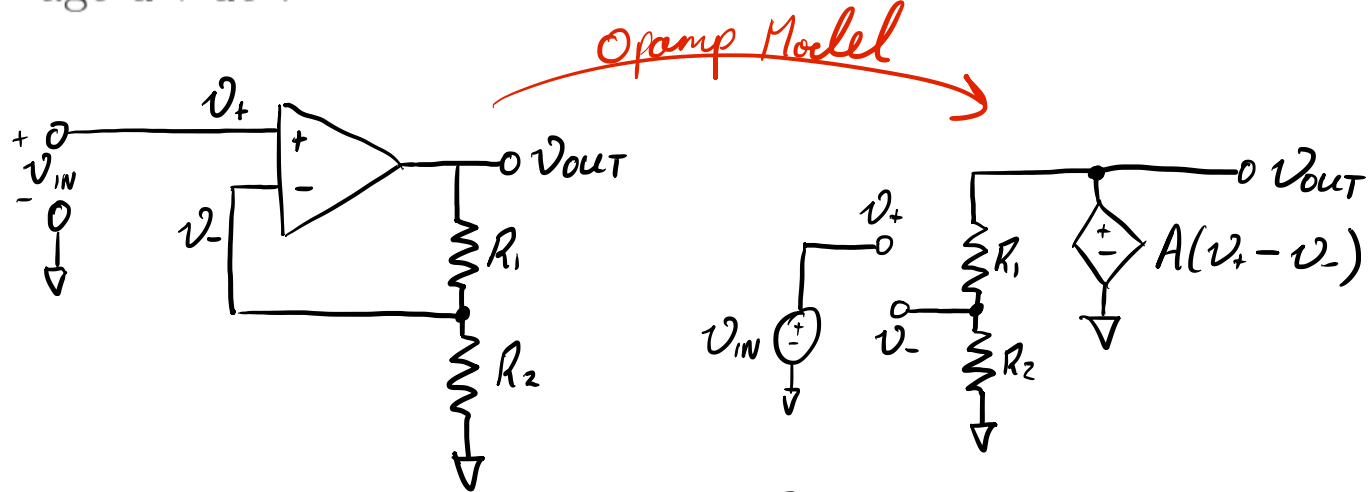

$$v_- = v_{OUT} \frac{R_2}{R_1 + R_2}$$

$$v_{OUT} = A \left(v_{IN} - v_{OUT} \frac{R_2}{R_1 + R_2} \right)$$


$$v_{OUT} = \frac{A(R_1 + R_2) v_{IN}}{R_1 + R_2 + AR_2} \approx v_{IN} \frac{A(R_1 + R_2)}{AR_2}$$

Consider the case of $A \gg 1$

$$v_{OUT} = \frac{R_1 + R_2}{R_2} v_{IN} = \left(1 + \frac{R_1}{R_2} \right) v_{IN}$$


If $R_1 = 47 \text{ k}\Omega$, and $R_2 = 10 \text{ k}\Omega$, the voltage gain is 5.7.

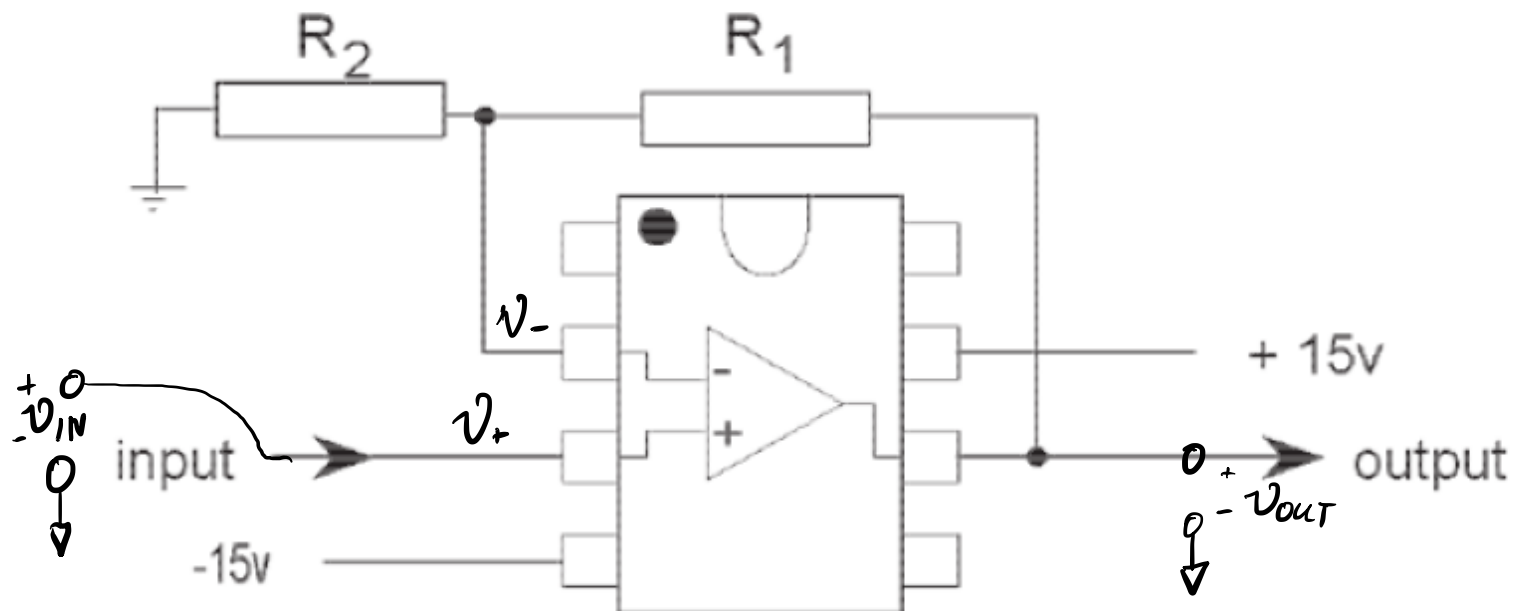The amplifier pinout arrangement is shown here for the 8-pin DIP:



6 Inverting Amplifier

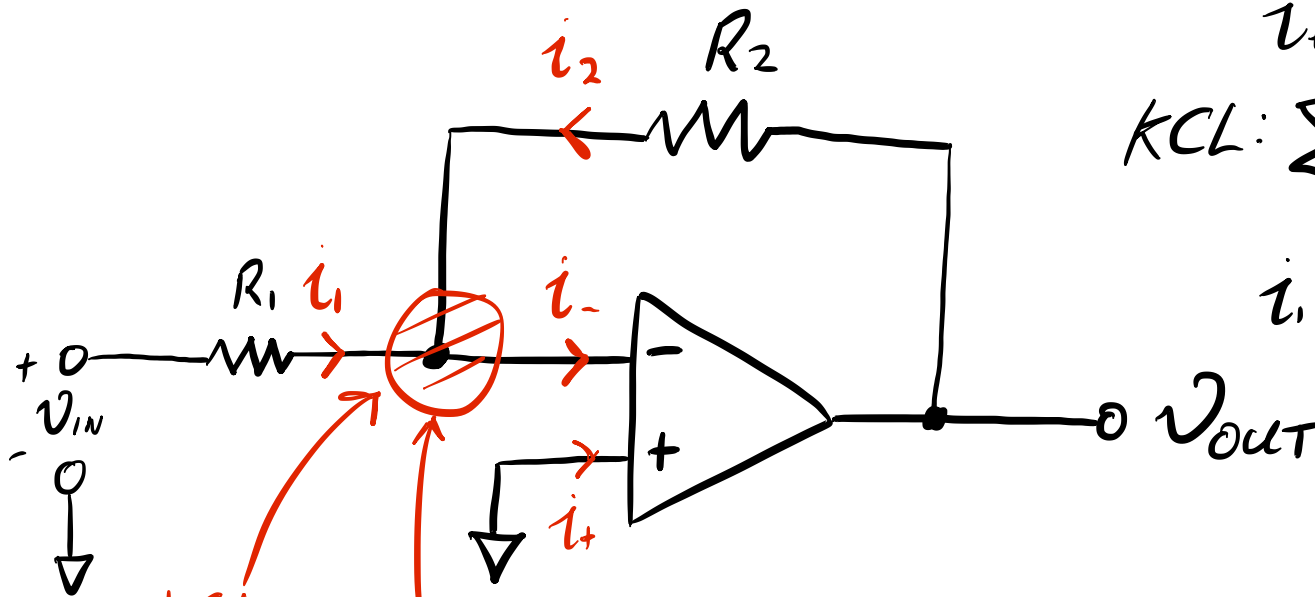The inverting amplifier has a configuration as shown below:



$$v_+ \approx v_- \approx 0$$

$$\text{KCL: } \sum i_{\text{IN}} - \sum i_{\text{OUT}} = 0$$

$$\downarrow$$
$$i_1 + i_2 = 0$$

KCL

Virtual ground

$v_- \approx v_+ \approx 0$
due to negative feedback

