

EE2013

NON-LINEAR CIRCUIT ANALYSIS

LECTURE 17: BASIC OPAMP CIRCUITS

Instructors: Alex Jaeger, Anthony Wall
Coordinator: Prof. Pádraig Cantillon-Murphy

LECTURE SCHEDULE

Thursdays 11am-1pm
(with short break)

Monday 9am-10am slot not used!

LECTURE NOTES

<https://www.jaeger.ie/ee2013/lec17>

Uploaded before lecture takes place

QUESTIONS?

Just ask whenever it comes to you!

OR:


anthony.wall@mcci.ie on Email, Teams or Canvas

1 Review from Last Time

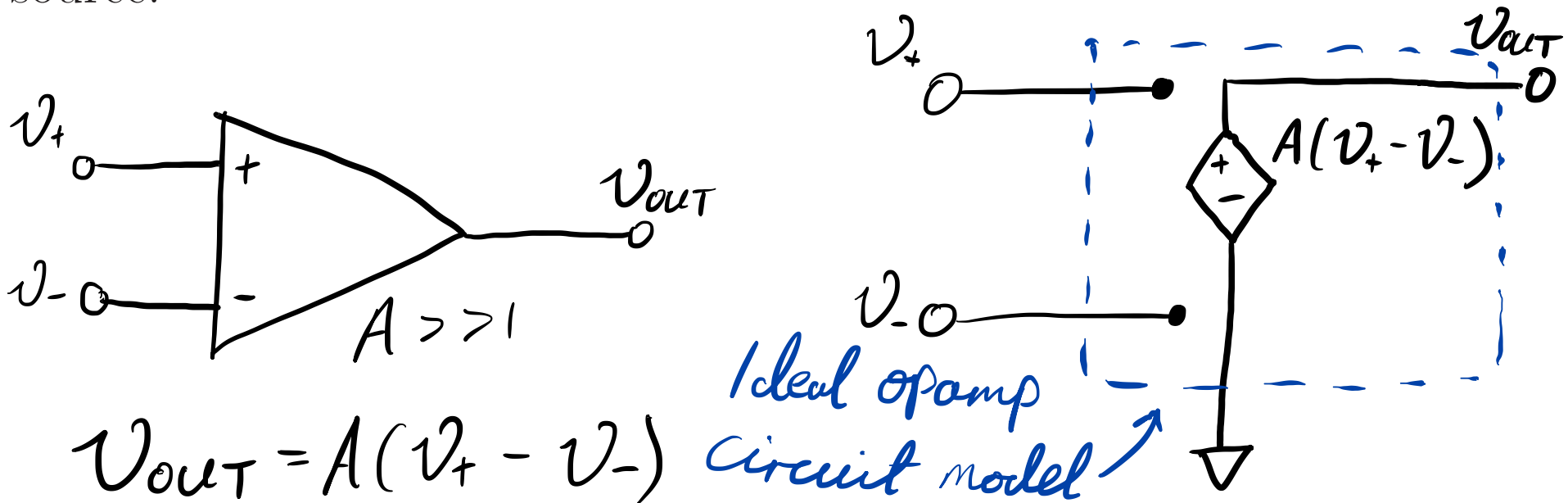1.1 Operational Amplifiers

The operational amplifier (op-amp) is a ubiquitous and very useful electronic component that enables the circuit designer to implement a large number of mathematical and logical functions (*e.g.*, addition, subtraction).

The circuit model for the op-amp is a high-gain, differential voltage source.




The analysis of op-amp circuits with NEGATIVE FEEDBACK is made significantly simpler by the following approximation which states that the positive and negative input terminal voltages of the op-amp are approximately equal in value.


$$v^+ \approx v^-$$

Using this approximation, we can find the input-output relation for a number of useful op-amp circuits.

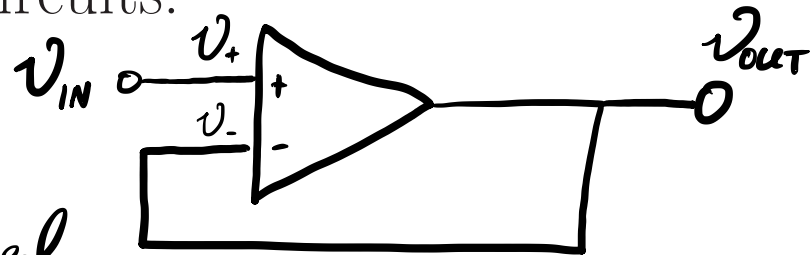If $v_+ \uparrow$ BUT: v_- Also \uparrow
Then $v_{out} \uparrow$ until $v_+ \approx v_-$
equilibrium is reached




1.2 Op-Amp Buffer

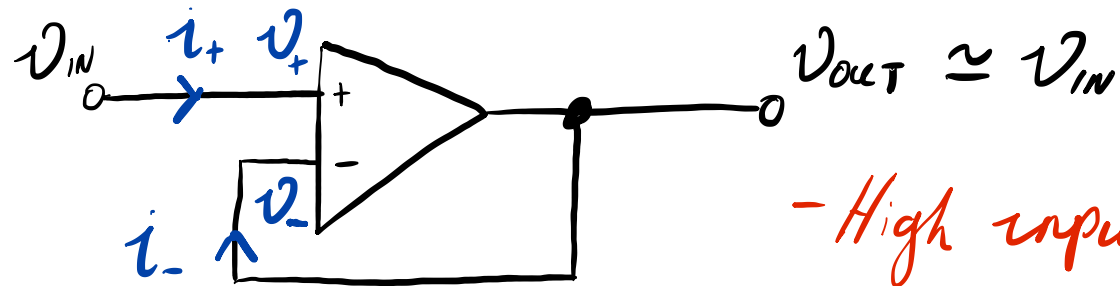

- High input impedance
- Low output impedance

1.3 Non-inverting Amplifier

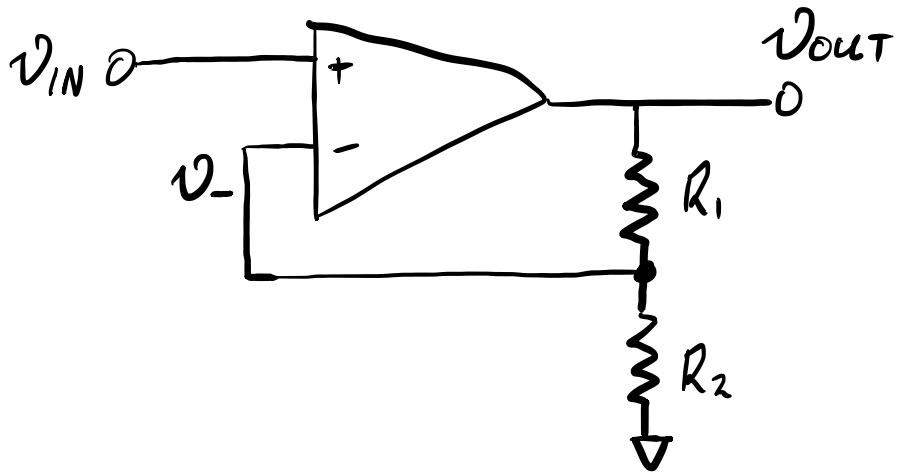


$$V_- = V_{OUT} \frac{R_2}{R_1 + R_2}$$

$$V_{OUT} = V_{IN} \left(1 + \frac{R_2}{R_1} \right)$$

Gain



1.4 Inverting Amplifier

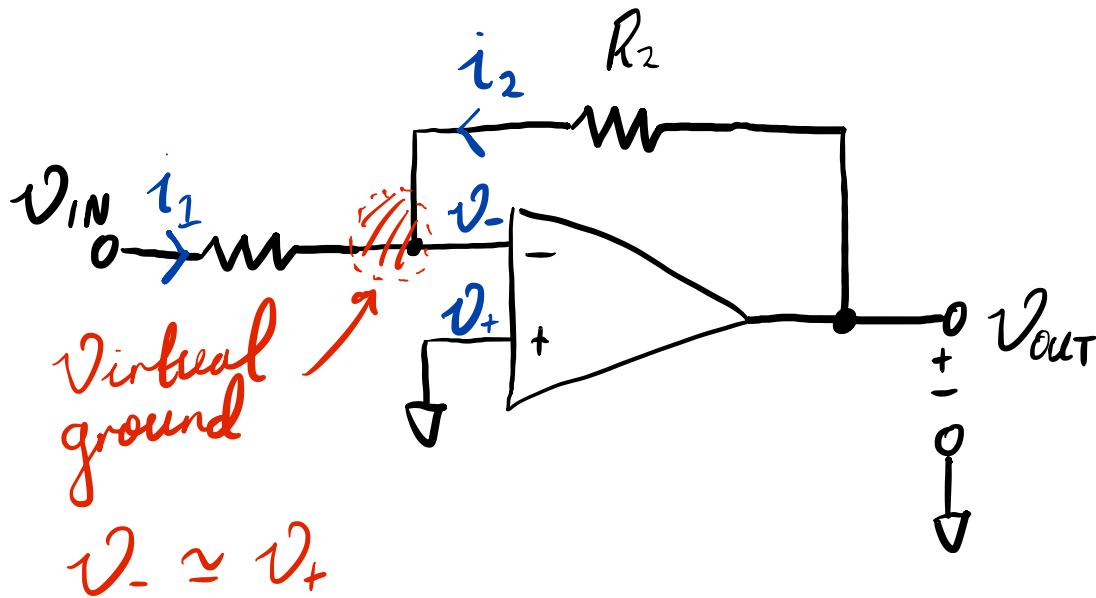

$$i_- \approx 0$$


$$i_1 + i_2 = 0$$

$$V_{OUT} \approx \left(\frac{-R_2}{R_1} \right) V_{IN}$$

180 deg Phase Shift

Gain

1.5 Op-Amp Adder

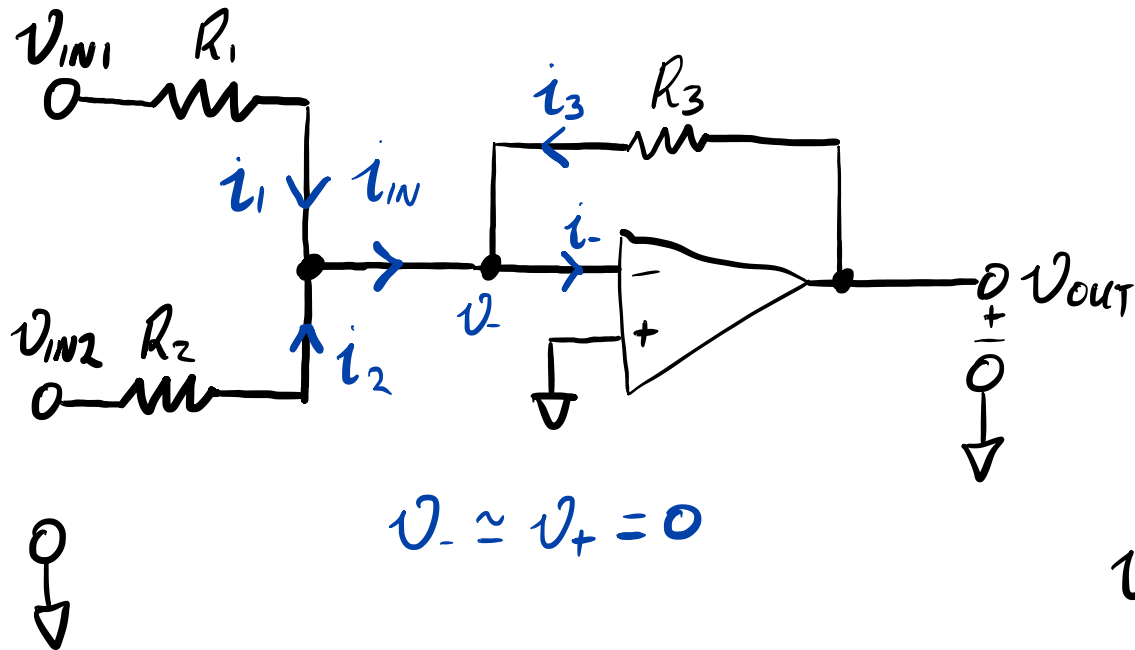

$$i_{IN} = i_1 + i_2$$

$$i_{IN} + i_3 = 0$$

↑
Same as inverting amp!


By Superposition:


$$V_{OUT} = V_{IN1} \left(\frac{-R_3}{R_1} \right) + V_{IN2} \left(\frac{-R_3}{R_2} \right)$$

2 Advanced Op-Amp Circuit Applications

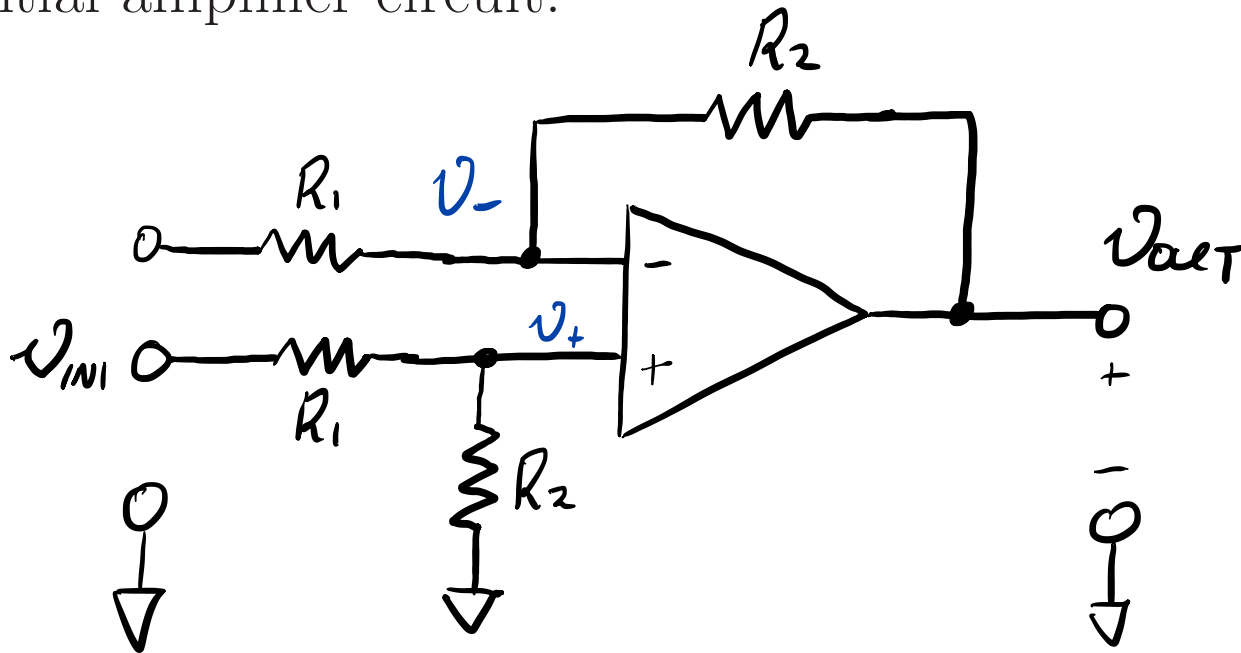2.1 Example 1: The Op-amp as a Differential Amplifier (Subtractor)

As we have already seen, the op-amp itself is essentially a differential amplifier. However, some modification is necessary to configure this differential gain to a designed value. The result is the differential amplifier circuit:



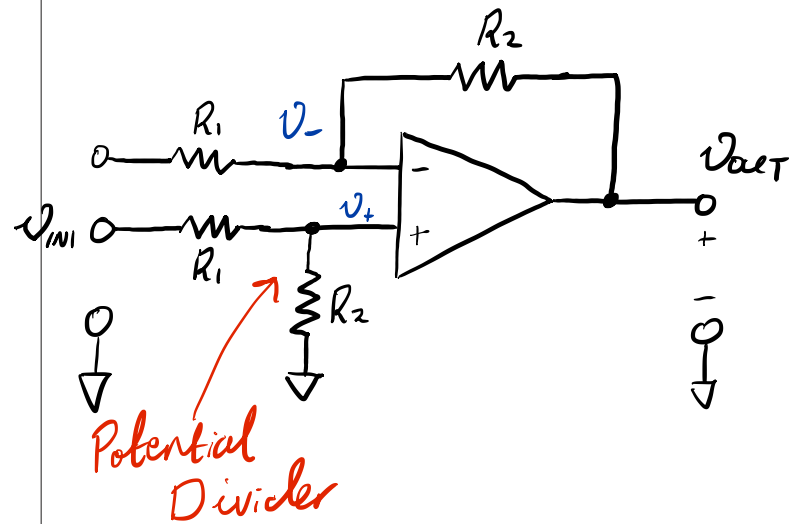


The analysis is simplified by the presence of negative feedback so that $v^+ \approx v^-$. The voltage at v^+ is given by potential division of v_1 :

$$v_+ = v_{in1} \left(\frac{R_2}{R_1 + R_2} \right)$$

$$v_- \approx v_+$$
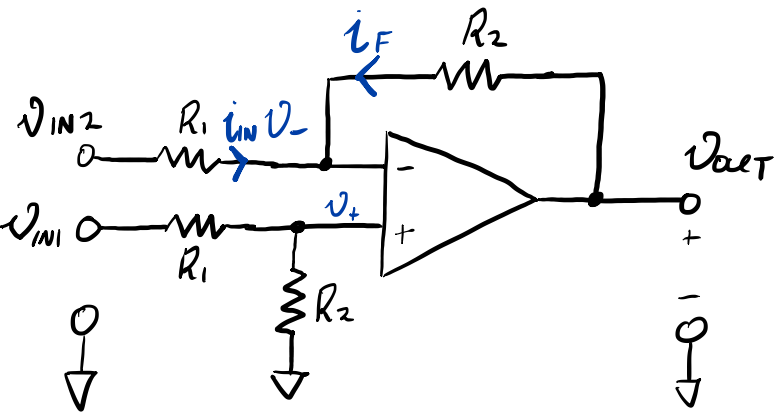
$$\hookrightarrow v_- \approx v_{in1} \left(\frac{R_2}{R_1 + R_2} \right)$$



This leads to the following expression for the current i_{in} :


$$i_{IN} = \frac{V_{IN2} - V_-}{R_1} \approx \frac{V_{IN2} - V_+}{R_1} = \frac{V_{IN2}}{R_1} - \frac{R_2 V_{IN1}}{R_1(R_1 + R_2)}$$

Similarly, i_F :

$$i_F = \frac{V_{OUT} - V_-}{R_1} \approx \frac{V_{OUT} - V_+}{R_1} = \frac{V_{OUT}}{R_2} - \frac{V_1 \cancel{R_2}}{\cancel{R_2}(R_1 + R_2)}$$

$$i_F = \frac{V_{OUT}}{R_2} - \frac{V_1}{R_1 + R_2}$$

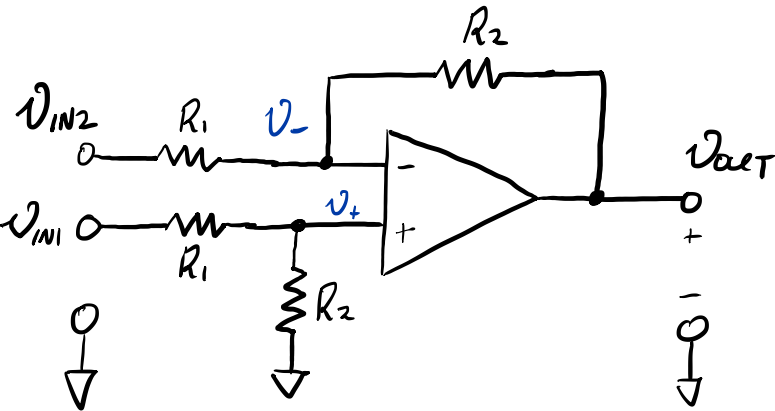Since no current flows into the input terminals of an ideal op-amp:



KCL: $i_F + i_{IN} = 0$

$$\frac{v_O}{R_2} - \frac{v_1}{R_1 + R_2} + \frac{v_2}{R_1} - \frac{v_1 R_2}{R_1(R_1 + R_2)} = 0$$

Gathering similar terms:

$$v_1 \left(\frac{R_2}{R_1(R_1 + R_2)} + \frac{1}{R_1 + R_2} \right) - v_2 \frac{1}{R_1} = \frac{v_O}{R_2}$$

Multiplying by R_1 :

$$v_1 \left(\frac{R_2}{R_1 + R_2} + \frac{R_1}{R_1 + R_2} \right) - v_2 = v_O \frac{R_1}{R_2}$$

This yields the characteristic input-output relation for the differential op-amp circuit:


$$v_{IN1} \left(\frac{R_2 + R_1}{R_1 + R_2} \right) - v_{IN2} = v_{OUT} \frac{R_1}{R_2}$$

$$v_{OUT} = \frac{R_2}{R_1} (v_1 - v_2)$$

Subtractor

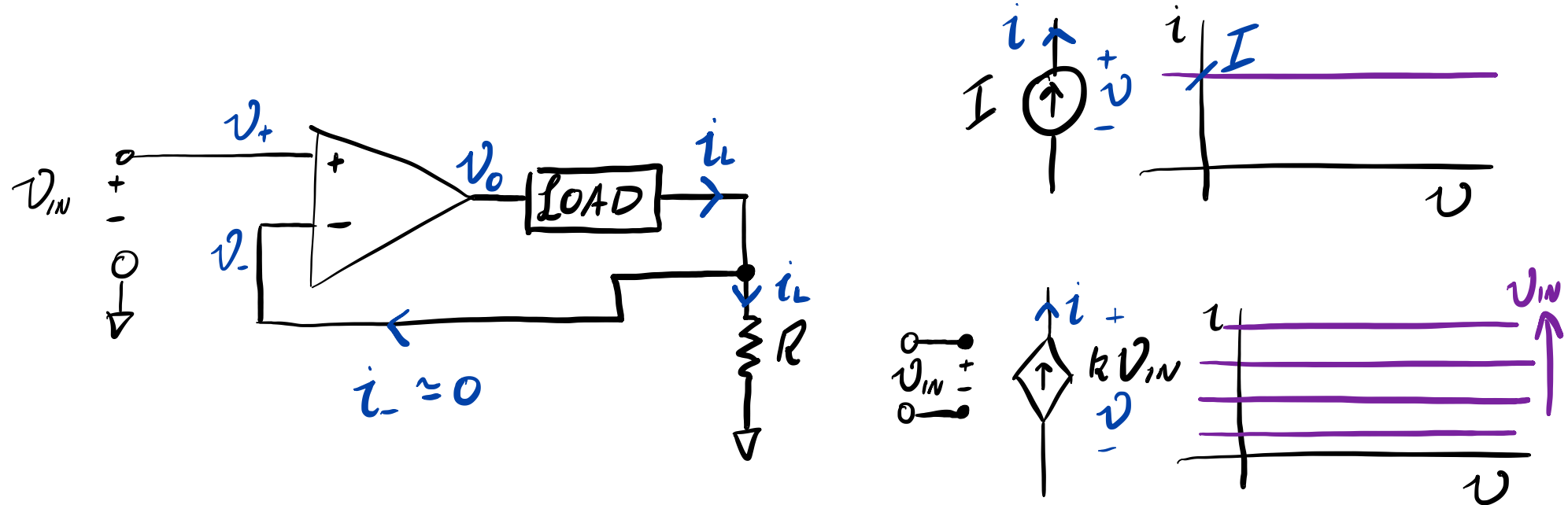2.2 Example 2: The Op-amp as a Current Source

A modification to the non-inverting amplifier configuration allows the op-amp to function as a voltage-controlled current source:



Assume that the op-amp drives a load of unknown resistance. A small resistor R , is placed in series with the load. Then the inverting input is $v^- = iR$. At the output of the amplifier:

$$v_o = A(v_+ - v_-)$$

$$v_o = A(v_{IN} - iR)$$


$$i = \frac{1}{R} \left(v_{IN} - \frac{v_o}{A} \right)$$

$$i = \frac{v_{IN}}{R}$$

i = Load current is independent of output voltage v_o and LOAD.


Its value depends on v_{IN}

⇒ Voltage Controlled Current Source

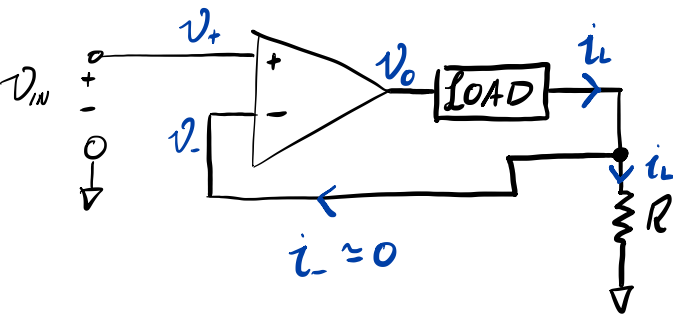

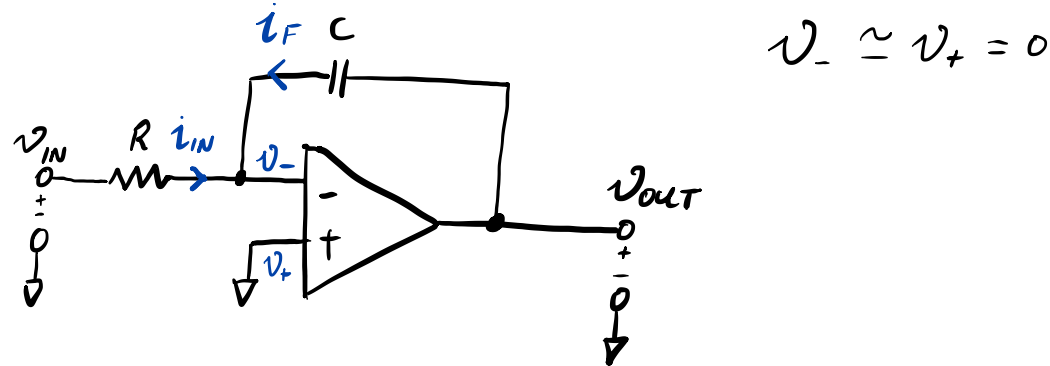2.3 Example 3: The Op-amp as an Integrator

If the feedback resistor in the inverting amplifier is replaced by a capacitor, C the amplifier becomes an integrator:



At the v^- terminal, we apply Kirchoff's current law as before but the feedback current is now defined by the elemental relationship for the capacitor:

$$i_{IN} + i_F = 0 \rightarrow KCL @ v_-$$

$$\frac{v_{IN} - v_-}{R} + C \frac{d(v_{OUT} - v_-)}{dt} = 0 \quad i_c = C \frac{dv_c}{dt}$$

$$\frac{v_{IN}}{R} + C \frac{dv_{OUT}}{dt} = 0$$

$$v_- \approx 0$$


$$v_o = -\frac{1}{RC} \int_0^t v_{IN}(t') dt' + v_c(0)$$

Initial Conditions

The result is a linear integration of the input voltage at the output.

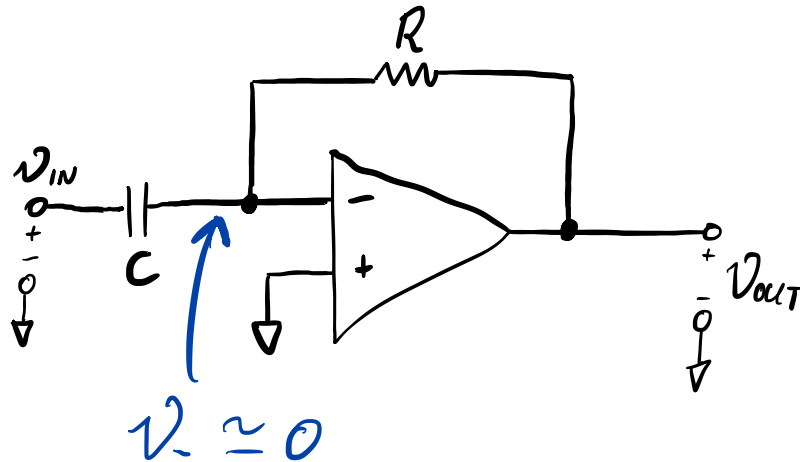2.4 Example 4: The Op-amp as a Differentiator


If the input resistor in the inverting amplifier is replaced by a capacitor, the circuit becomes a differentiator:



At the v^- terminal, we apply Kirchoff's current law as before but the input current is now defined by the elemental relationship for the capacitor:

$$i_{IN} + i_F = 0$$
$$C \frac{dv_{IN}}{dt} + \frac{v_{OUT}}{R} = 0$$
$$i_C = C \frac{dv_C}{dt}$$
$$\Rightarrow v_{OUT} \approx -RC \frac{dv_{IN}}{dt}$$

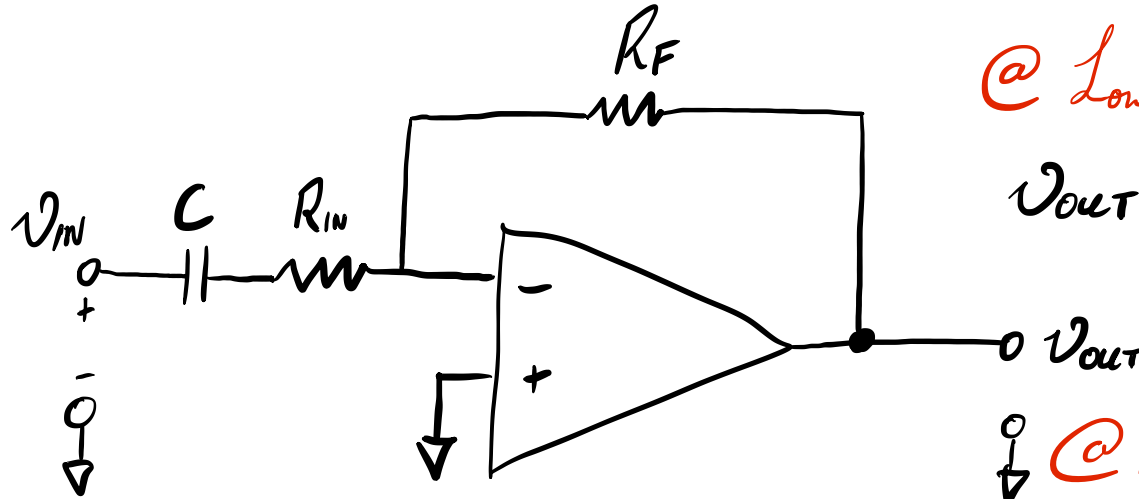Design Note: While the op-amp differentiator circuit is easily implemented, pure differentiators are rarely used because of their susceptibility to electrical noise. In practice, it is common to put a resistor in series with the capacitor to alleviate this issue.



@ Low frequencies :

$$V_{OUT} \approx -R_F C \frac{dV_{IN}}{dt}$$

@ High frequencies :

$$V_{OUT} \approx \frac{R_F}{R_{IN}} V_{IN}$$

